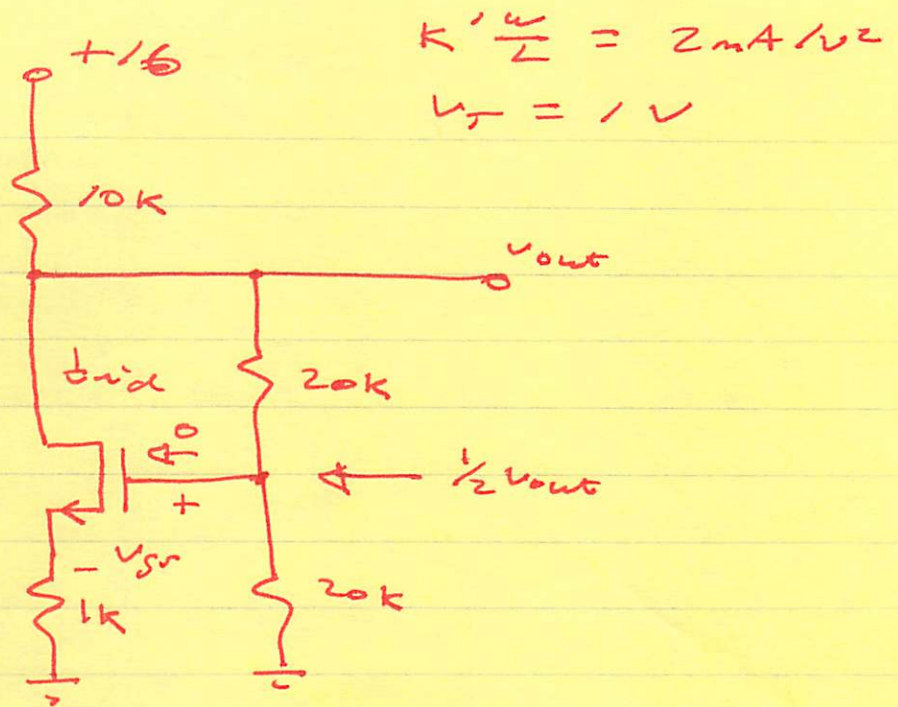


11.10

a)

Drawing
circuit



$$\frac{V_{out}}{40} + i_d = \frac{16 - V_{out}}{10}$$

$$\begin{aligned} \hookrightarrow V_{out} + 40 i_d &= 64 - 4 V_{out} \\ 5 V_{out} &= 64 - 40 i_d \end{aligned}$$

$$\begin{aligned} V_{gs} &= \frac{1}{2} V_{out} - i_d (1) \\ 10 V_{gs} &= 5 V_{out} - 10 i_d = 64 - 50 i_d \\ V_{gs} &= 6.4 - 5 i_d \end{aligned}$$


$$\text{sat. } i_d = \frac{1}{2} (2) (V_{gs} - 1)^2 = (V_{gs} - 1)^2$$

$$\begin{aligned} V_{gs} &= 6.4 - 5 V_{gs}^2 + 10 V_{gs} - 5 \\ 5 V_{gs}^2 - 9 V_{gs} - 1.4 &= 0 \end{aligned}$$

$$V_{gs} = \frac{9 \pm \sqrt{81 + 28}}{10} = 1.94 \text{ V}, -0.14 \text{ V}$$



$$i_d|_Q = (1.94 - 1)^2 = 0.884 \text{ mA}$$

b)

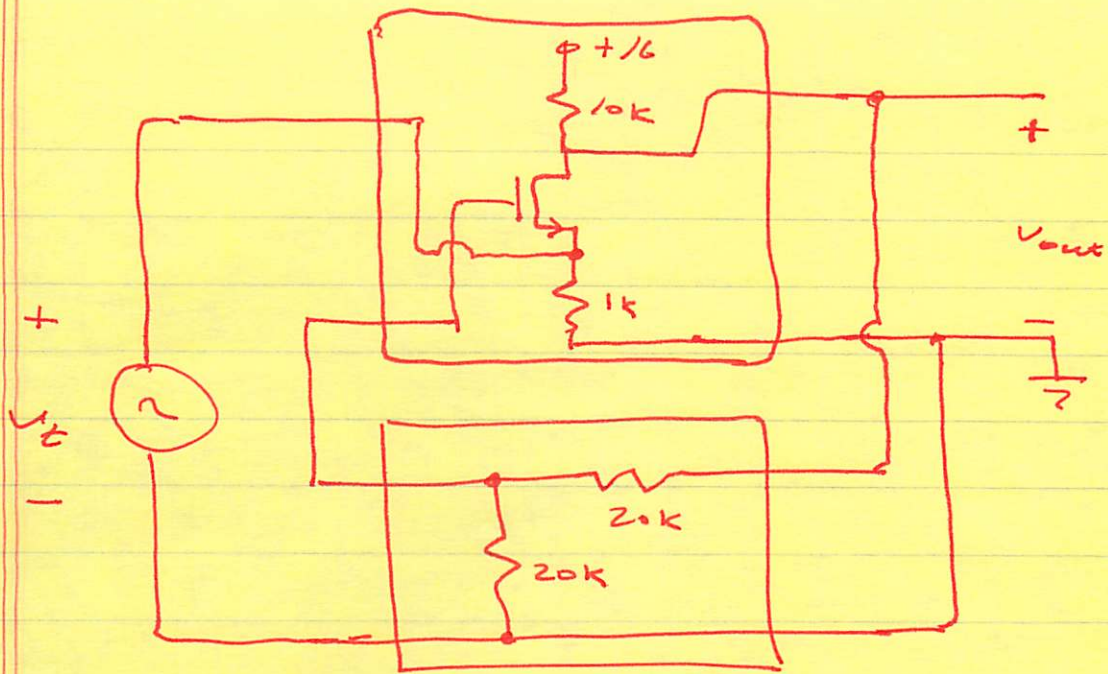


c)

loading from feedback:

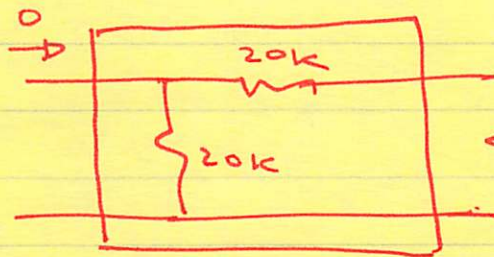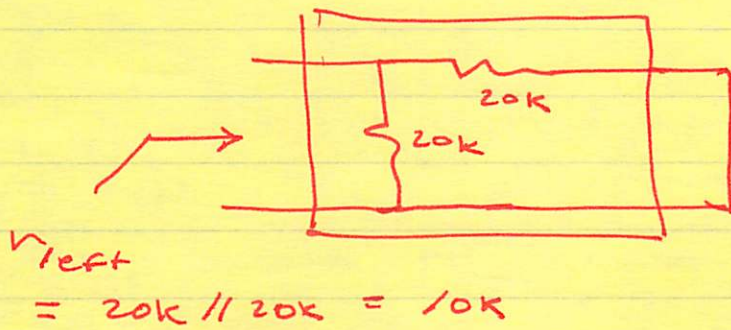

$$V_{right} = 20k + 20k = 40k$$

"a" circuit

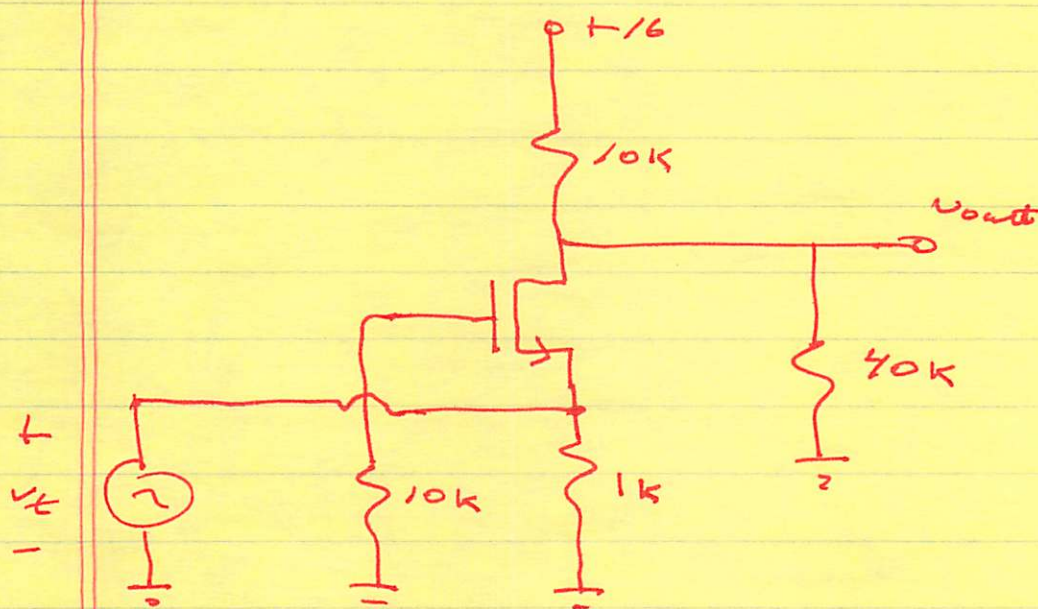

Common source: $\frac{v_{out}}{v_t} = g_m (10k \parallel 40k)$

$$g_m = \sqrt{2 \mu_{eff} k' \frac{W}{L}} = \sqrt{2 \times 0.884 \text{ mA} \times 2 \frac{\text{mA}}{\text{V}^2}} = 1.88 \times 10^{-3} \text{ V}$$

$$a = 1.88 \times 10^{-3} \text{ V} \times 8 \times 10^3 \Omega = 15$$





$$f = \frac{v_1}{v_2} = \frac{1}{2}$$

so with feedback

$$\frac{v_{out}}{v_t} = \frac{a}{1 + af} = \frac{15}{1 + 15(0.5)} = \underline{1.77}$$

11.20

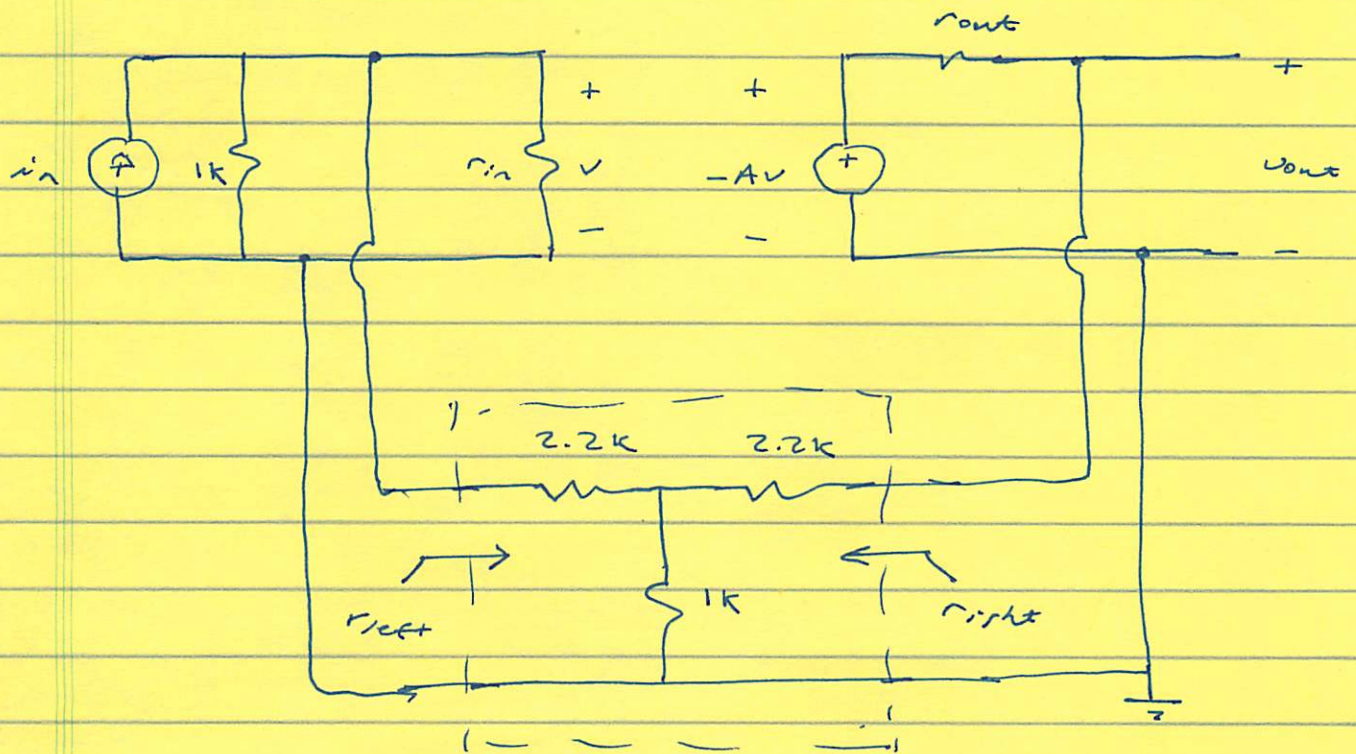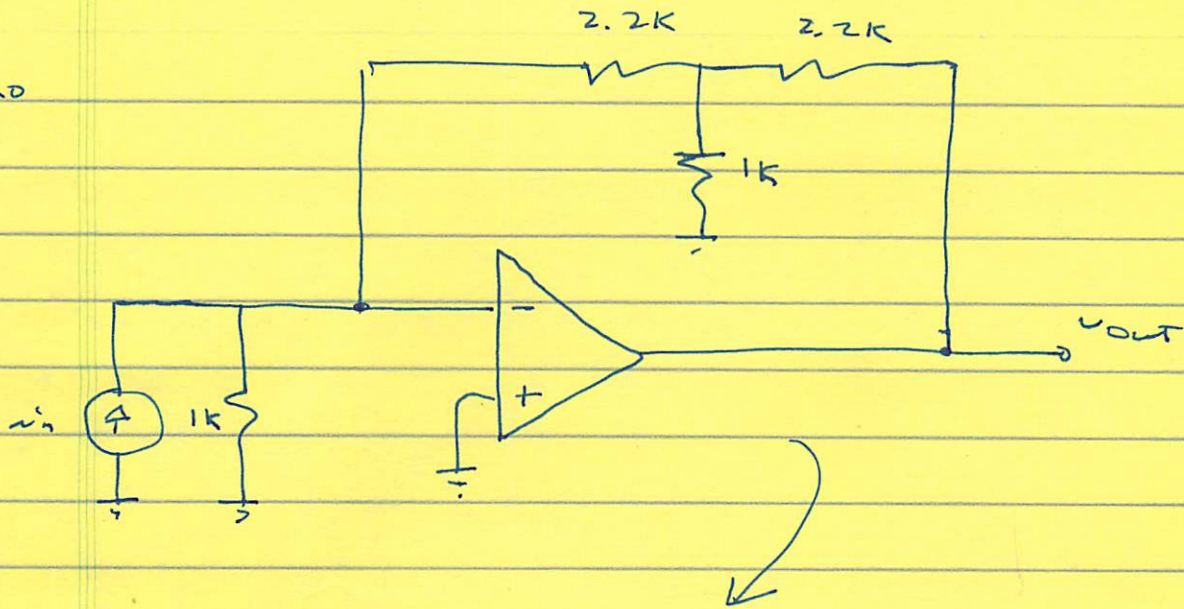

$$r_{in} = 400k$$

$$r_{out} = 80\Omega$$

$$A = 100,000$$


$$r_{left} = r_{right} = 2.2k + 1k // 2.2k = 2.89k$$

(opposite side shorted, shared voltage)

$$\frac{V}{v_n} = 1k \parallel 2.89k \parallel 400k = 742 \Omega$$

$$v_{out} = -A_v \frac{2890}{2890 + 80} = -97,300 V$$
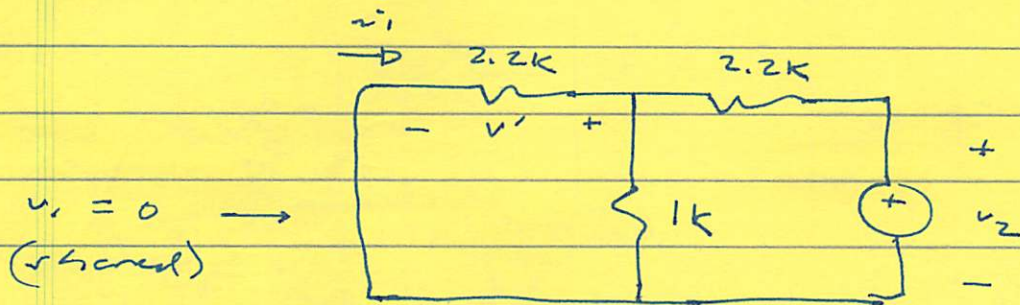
$$\frac{v_{out}}{v_n} = \frac{v_{out}}{V} \frac{V}{v_n} = -7.22 \times 10^7 \Omega = a$$



$$f = \frac{v_1}{v_2}$$

$$v' = v_2 \frac{2.2k \parallel 1k}{2.2k \parallel 1k + 2.2k} = 0.278 v_2$$

$$-v_1 = \frac{0.278 v_2}{2.2k} = -1.08 \times 10^{-4} v_2$$

$$f = -1.08 \times 10^{-4} v$$

With feedback,


$$\begin{aligned} \frac{v_{out}}{v_n} &= \frac{a}{1 + af} = \frac{-7.22 \times 10^7 \Omega}{1 + (-7.22 \times 10^7)(-1.08 \times 10^{-4})} \\ &= -9260 \Omega \end{aligned}$$

12.12


$$A_0 = 1200 \quad F = 1$$

$$A_0 F = 1200 = 61.6 \text{ dB}$$

$|AF|_{\text{dB}}$

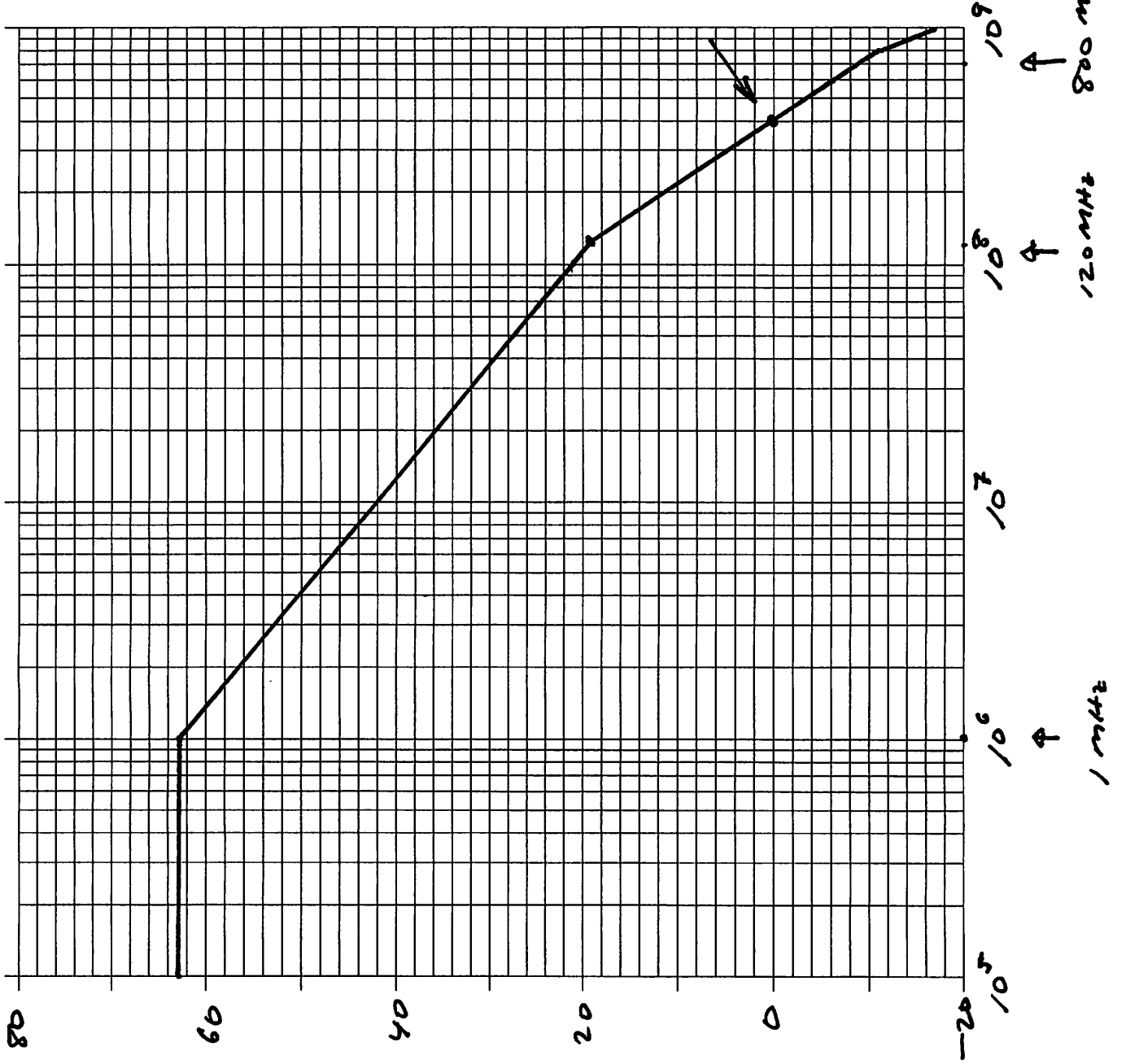

$|AF| = 1$
at $f_T \approx 400 \text{ MHz}$

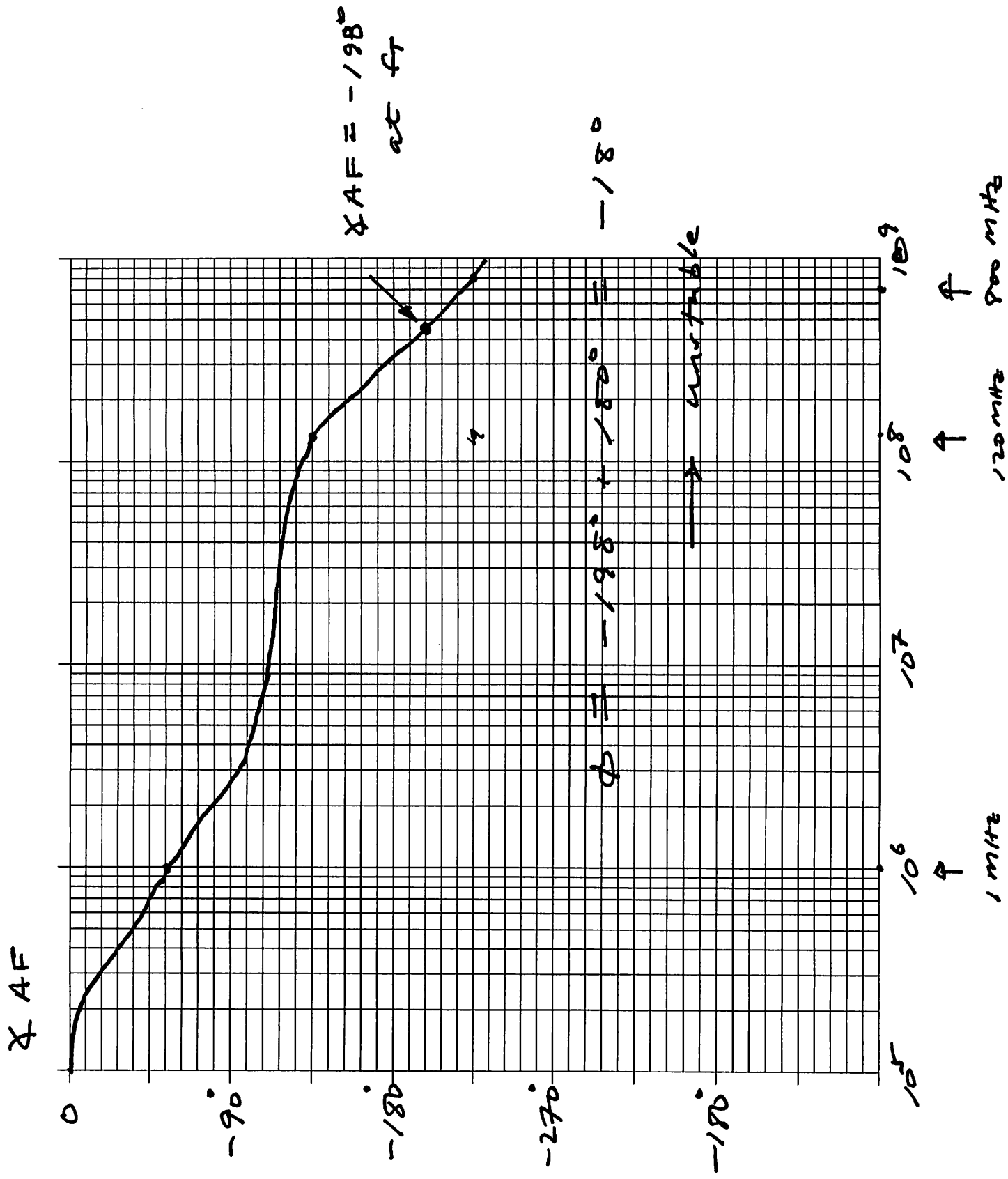

12.33

$$A_0 = 25,000$$

Let $F = 1$ (worst case)

$$f_{p1} = 2 \text{ MHz}, f_{p2} = 10 \text{ MHz}, f_{p3} = 80 \text{ MHz}$$

$$\text{want } \phi = 60^\circ$$

$$f_T = 2 \text{ MHz} \tan(90^\circ - 60^\circ) = 1.16 \text{ MHz}$$

$$f_{po} = \frac{1.16 \text{ MHz}}{\underbrace{25,000}_{A_0 F} \cos(90^\circ - 60^\circ)} = 54 \text{ Hz}$$