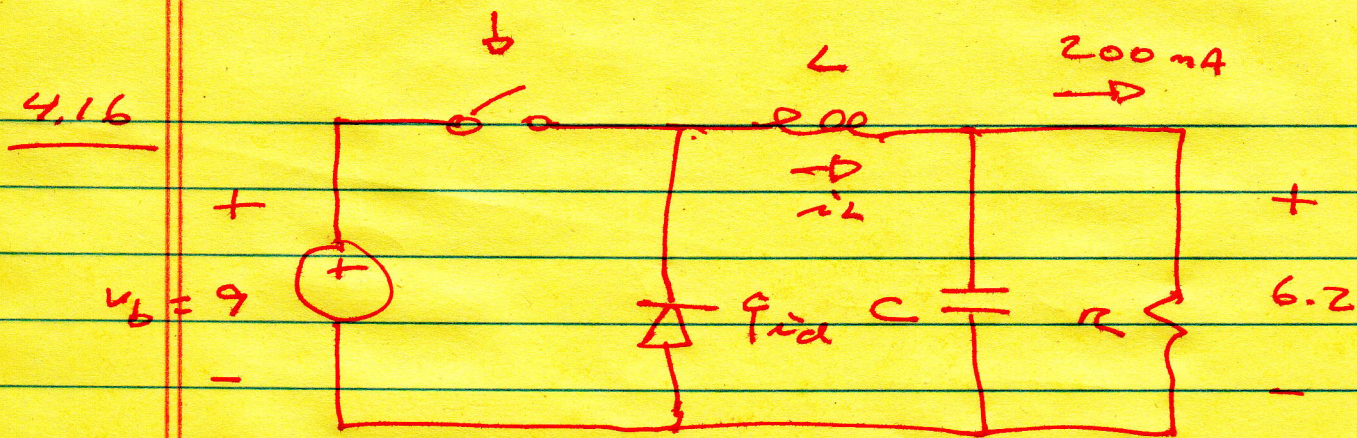


$$f = 180 \text{ kHz}$$



$$V_{\text{ripple}} < 0.2 \text{ V}$$

$$R = \frac{6.2}{0.2} = 31 \Omega$$

$$D = \frac{6.2}{9} = 0.69$$

$$L > \frac{V_b (1-D) DT}{2 \times \text{dc load current}}$$

$$= \frac{9(0.31)(0.69)}{0.4 \times 180 \times 10^3} = 26.7 \mu\text{H}$$

→ choose 33 μH

$$RC \sim 10T \rightarrow C = \frac{10}{31 \times 180 \times 10^3}$$

$$= 1.79 \mu\text{F}$$

→ choose 2.2 μF

$$i_{L,p-p} = \frac{V_b (1-D) DT}{L} = 0.32 \text{ A}$$


$$\rightarrow ESR < \frac{0.2}{0.32} = 0.63 \Omega$$

$$I_d(\text{max}) = i_L(\text{max}) = 200 \text{ mA} + 320 \text{ mA} = 520 \text{ mA}$$

→ 1-A diode good

4.24) Design boost converter that delivers 60 mA at 8V from a 4.5-V dc source. Use the MAX 1790 controller at 640 kHz. Specify pin connections.

easy filtering
faster loop performance

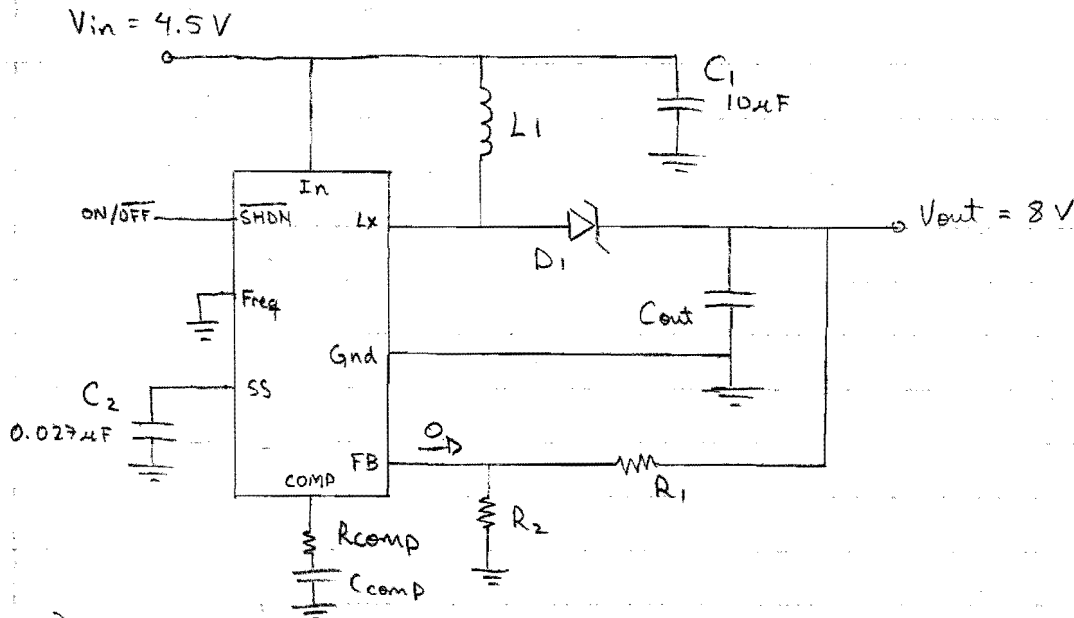

a)

$$L = \left(\frac{V_{in}}{V_{main}} \right)^2 \left(\frac{V_{main} - V_{in}}{I_{main(max)} \cdot f_{osc}} \right) \left(\frac{n_{typ}}{LIR} \right)$$

$$= \left(\frac{4.5}{8} \right)^2 \left(\frac{8 - 4.5}{(0.06)(640000)} \right) \left(\frac{0.87}{0.5} \right)$$

$$= 50.180054 \mu H \approx 51 \mu H$$

$$I_{in(DC, Max)} = \frac{I_{main(max)} \cdot V_{main}}{V_{in(min)} \cdot \eta_{min}} = \frac{0.06 \cdot 8}{4.5 \cdot 0.87} = 0.122605 A$$

$$I_{ripple} = \frac{V_{in(min)} \cdot (V_{main} - V_{in(min)})}{L \cdot V_{main} \cdot f_{osc}} = \frac{4.5(8 - 4.5)}{(51 \times 10^{-6}) 8(640 \times 10^3)} = 0.06032 A$$

$$I_{peak} = I_{in(DC, max)} + \frac{I_{ripple}}{2} = 0.1528 A$$

series resistance of inductor $\rightarrow 0.1 \Omega$

$$\therefore C = \frac{0.5 \cdot L \cdot (I_{peak})^2}{V_{ripple} \cdot V_{out}} = \frac{(0.5)(51 \times 10^{-6})(0.1528^2)}{(0.06032) \cdot (8)} = 12.09 \mu F \rightarrow 15 \mu F$$

$$V_{ripple} = I_{ripple} \cdot 0.1 \Omega$$

ESR

$$R_1 = R_2 \left(\frac{V_{out}}{V_{FB}} - 1 \right)$$

$$V_{FB} = 1.24V$$

standard value

So can choose $R_1 = 110 k\Omega$

$$R_2 = 20 k\Omega$$

$$R_{comp} = \left(200 \frac{\Omega}{A^2} \right) (V_{out})^2 \left(\frac{C_{out}}{L} \right)$$

$$= 200 (8)^2 \left(\frac{15}{51} \right) = 3.765 \text{ K}\Omega \rightarrow 3.6 \text{ K}\Omega$$

$$C_{comp} = \left(0.4 \times 10^{-3} \frac{A}{\Omega} \right) \left(\frac{L}{V_{in}} \right)$$

$$= (0.4 \times 10^{-3}) \left(\frac{51 \times 10^{-6}}{4.5} \right) = 4.53 \times 10^{-9} \rightarrow 470 \text{ pF}$$

b) Based on the graphs for the typical operating characteristics of the MAX 1790 (page 5 of datasheet), the efficiency is approximately 87 %.


c) Cost Analysis

Component Type	Digi-key part number	Manufacturer part number	Description	Manufacturer	Price (1000 components)
Capacitor C _{out}	399 3298 2 ND	C1210C156K8PACTU	CAP ceramic 15uF 10V X5R 1210	Kemet	\$ 221
Resistor R ₁	218794953 ND	218794953	RES 110K OHM 1/5W 5% 0603	TE connectivity	\$ 2.9
Resistor R ₂	18794955 ND	1879495-5	RES 20.0K OHM 1/5W 5% 0603	TE connectivity	\$ 2.9
Capacitor C ₁	1812YC106JAT2A ND	1812YC106JAT2A	CAP CER 10uF 16V 5% X7R 1812	AVX corporation	\$ 490
Capacitor C ₂	478 1168 1 ND	06035A270JAT2A	CAP CERM 27pF 5% 50V NPO 0603	AVX corporation	\$ 61
Diode D ₁	FL28V2BTR ND	FL28V2B	Diode Zener 8.2V 500 MW SOD-80	Fairchild Semiconductor	\$ 49
Inductor L ₁	ASPI60455510MTND	ASPI60455510MT	Inductor Power 51uH SMD	Abracon Corporation	\$ 225
Resistor R _{comp}	818794946 ND	818794946	RES 3.60K OHM 1/5W 5% 0603	TE connectivity	\$ 2.9
Capacitor C _{comp}	478 6201 1 ND	06033A471JAT2A	CAP CER 470pF 25V NPO 0603	AVX corporation	\$ 77
					<u>\$ 1131.70</u>

Add Max1790 component

4.29

a)

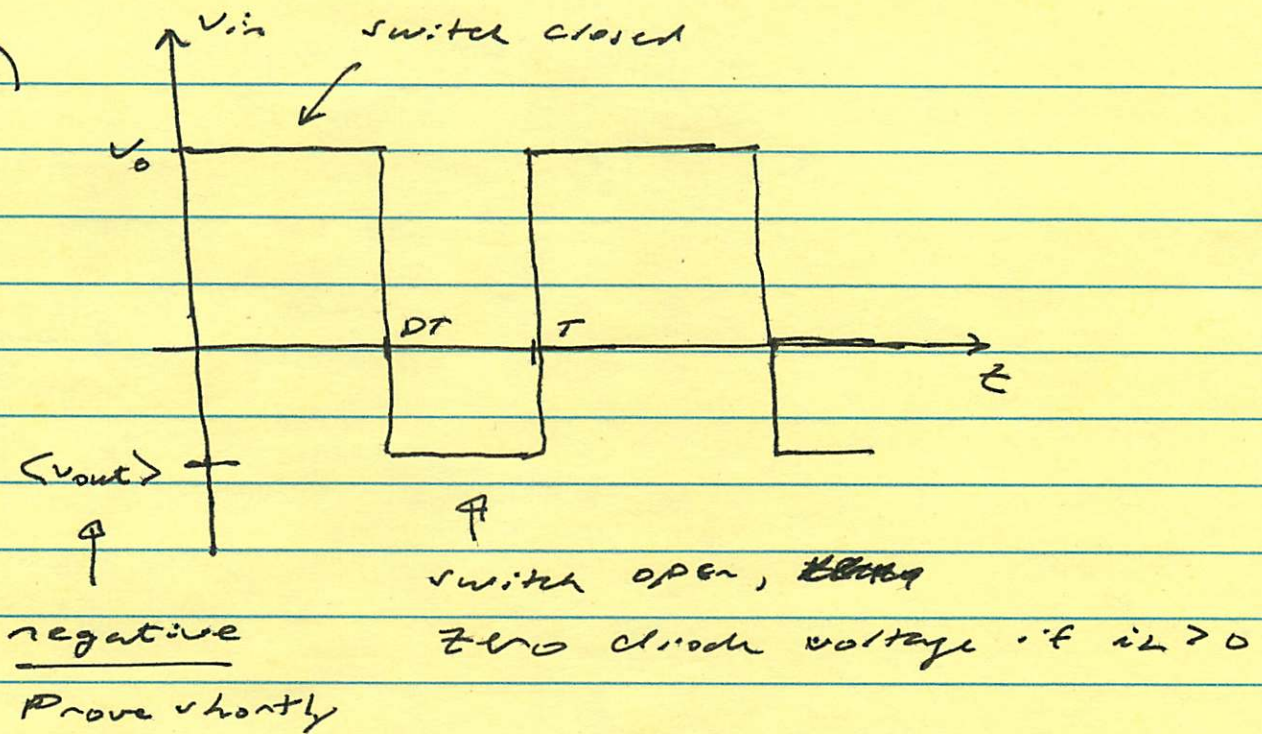


$$b) \langle v_L \rangle = \langle v_{in} \rangle = 0$$

$$0 = \frac{1}{T} [V_o DT + \langle v_{out} \rangle (1-D)T]$$

$$\rightarrow v_{out} = \frac{-DV_o}{1-D}$$

c) switch closed

$$L \frac{di_L}{dt} = V_o$$

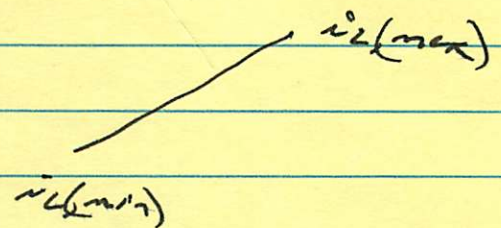

$$i_L(max) - i_L(min) = \frac{V_o DT}{L}$$

4.29
(cont.)

$$\text{Inductor energy stored} = \frac{1}{2} L i_{L(\max)}^2 - \frac{1}{2} L i_{L(\min)}^2$$

$$= \frac{1}{2} \left[\frac{-DV_0}{1-D} \right]^2 DT$$

$\underbrace{\hspace{10em}}_{\text{Load Power}} \quad \underbrace{\hspace{10em}}_{\text{switch closure time}} \quad \frac{V_0 DT}{2}$

$$\left(\frac{1}{2} L \right) (i_{L(\max)} - i_{L(\min)}) (i_{L(\max)} + i_{L(\min)})$$

$$= \frac{DT}{2} \frac{D^2 V_0^2}{(1-D)^2}$$

$$i_{L(\max)} + i_{L(\min)} = \frac{2 V_0 D^2}{2L(1-D)^2}$$

$$i_{L(\max)} - i_{L(\min)} = \frac{V_0 DT}{2L}$$

$$i_{L(\max)} = \frac{V_0 D^2}{2L(1-D)^2} + \frac{V_0 DT}{2L}$$

d) $i_{L(\min)} > 0$

$$\hookrightarrow L > \frac{RT(1-D)^2}{2D} = \frac{R}{2} DT \left(\frac{V_0}{V_{out}} \right)^2$$

e) $RC \gg T$