

5.2.6


$$K_p' = 20 \text{ mA/V}^2$$

$$V_{TH} = -0.6 \text{ V}$$

$$V_{in} = 0 \text{ (Low)} \rightarrow V_{out} = 3.1 \text{ V}$$

$$3.3 \frac{R}{R + r_{ds}} = 3.1$$
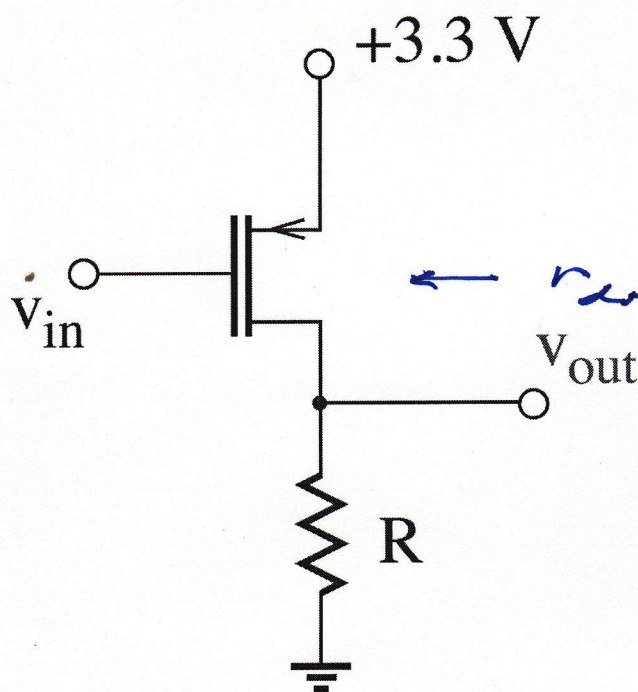
$$\text{Power} \rightarrow \frac{(3.1)^2}{R + r_{ds}} = 0.5 \quad (\text{kHz resistors})$$



$$R + r_{ds} = \frac{21.78}{0.5} \text{ k} = 43.56 \text{ k}$$

$$R = \frac{3.1}{3.3} \times (43.56) = 40.92 \text{ k}$$

$$\rightarrow r_{ds} = 1.72 \text{ k}$$

$$\frac{1}{r_{ds}} = K_p' \left(\frac{W}{L} \right) |V_{GS} - V_{TH}|$$

$$\frac{W}{L} = \frac{1}{r_{ds} \times K_p' \times |V_{GS} - V_{TH}|}$$

$$= \frac{1}{1.72 \frac{\text{V}}{\text{mA}} \times 0.02 \text{ mA/V}^2 \times |-3.3 + 0.6| \text{ V}}$$
$$= 14$$

5.29


$$K_n' = 50 \mu\text{A/V}^2$$

$$V_T = 0.6 \text{ V}$$

$$V_K = 5 \text{ V}$$

$$\frac{r_{ds}}{r_{ds} + 4 \text{ k}} = 0.1 \rightarrow r_{ds} = 0.444 \text{ k}$$

attenuation
factor

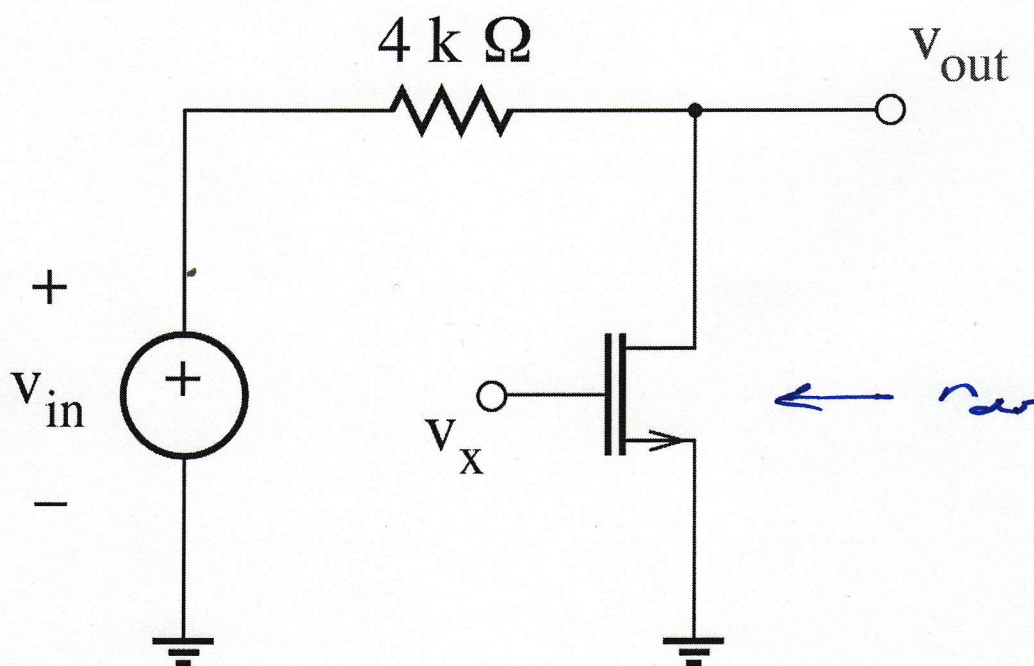

$$\frac{1}{r_{ds}} = K_n' \left(\frac{W}{L} \right) (V_{GS} - V_T)$$


$$\left(\frac{W}{L} \right) = \frac{1}{0.444 \frac{\text{mA}}{\text{V}} \times 0.05 \frac{\text{mA}}{\text{V}^2} \times (5 - 0.6)}$$

$$= \underline{\underline{10.2}}$$

$$K' \frac{W}{L} = 0.5 \text{ mA/V}^2$$

$$V_T = 1 \text{ V}$$

$$5.42$$

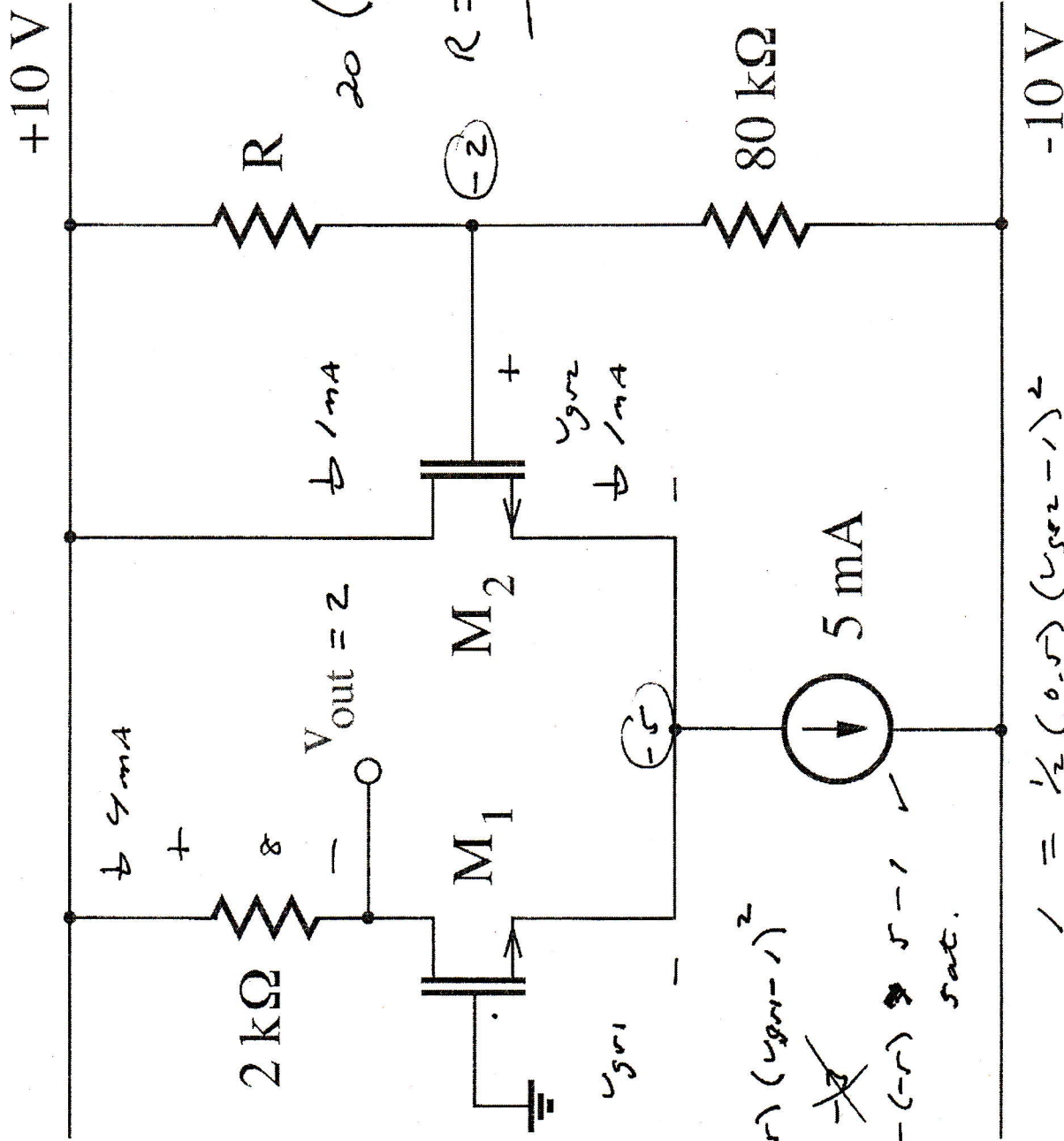

$$R = 20 \left(\frac{80}{80 + n} \right) = 120 \text{ k}\Omega$$

$$I = \frac{1}{2} (0.5) (V_{gs1} - 1)^2$$

$$V_{gs1} = 5, \text{ sat.}$$

$$V_{ds1} = 10 - (-5) = 15 \text{ V}$$

$$I = \frac{1}{2} (0.5) (V_{gs2} - 1)^2$$

$$V_{gs2} = 3, \text{ sat.}$$


$$V_{ds2} = 10 - (-5) = 15 \text{ V}$$

5.43

$$K' \frac{W}{L} = 1 \text{ mA/V}^2, \quad V_T = 1 \text{ V}$$

$$M_2 \rightarrow 2 = \frac{1}{2} (1) (V_{DS2} - 1)^2 \rightarrow V_{DS2} = 3 \text{ V}$$

$$V_{GS2} = -1 \text{ V}$$

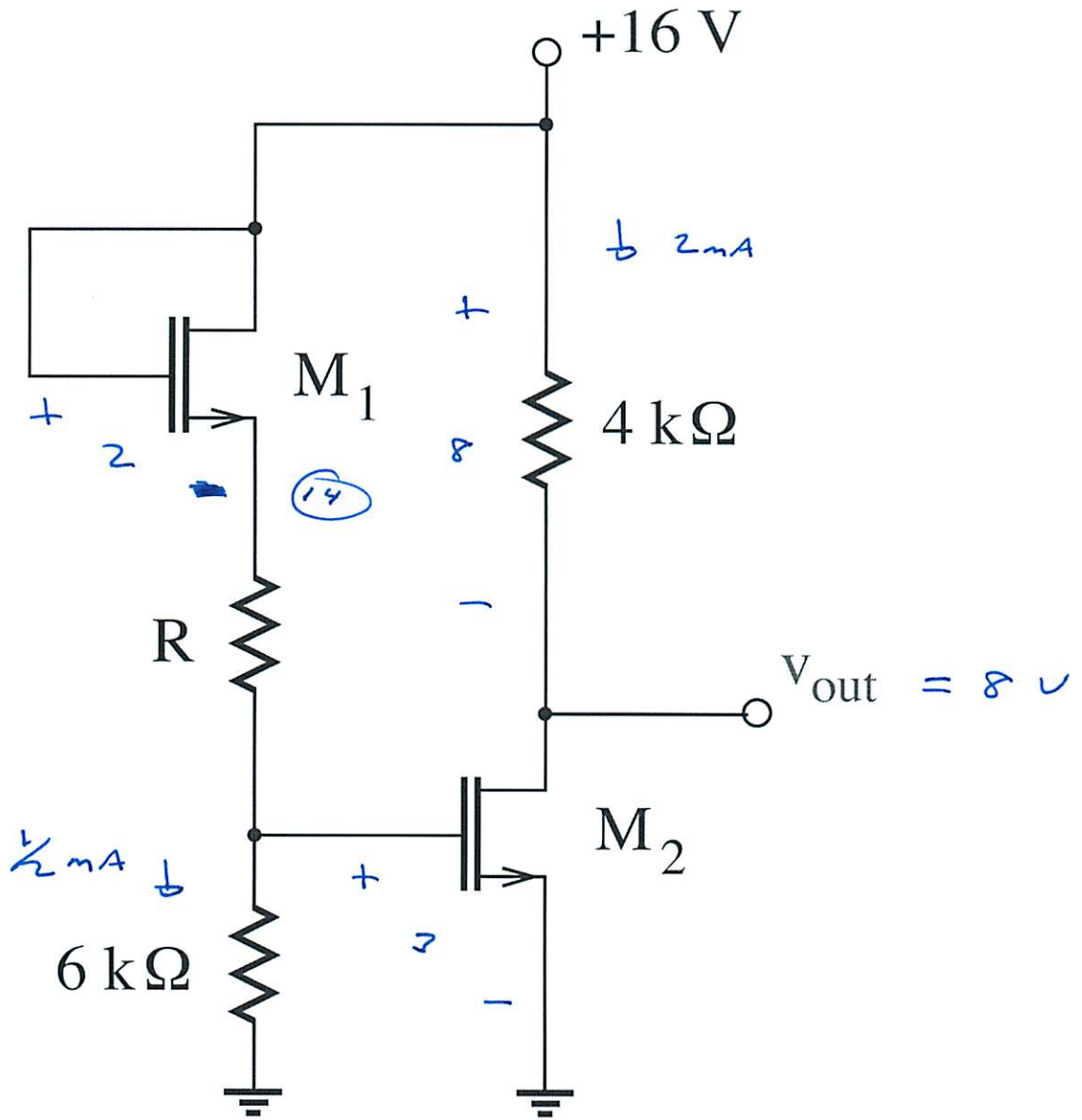

$$M_1 \rightarrow \frac{1}{2} = \frac{1}{2} (1) (V_{GS1} - 1)^2 \rightarrow V_{GS1} = 2 \text{ V}$$

$$V_{DS1} = 0 \text{ V}$$


$$R = \frac{14 - 3}{0.5} = 22 \text{ k}\Omega$$

5.45

$$M_1 : K_n' \frac{W}{L} = 2 \text{ mA/V}^2 \quad V_T = 1 \text{ V}$$

$$M_2 : K_p' \frac{W}{L} = 0.25 \text{ mA/V}^2 \quad V_T = -1 \text{ V}$$
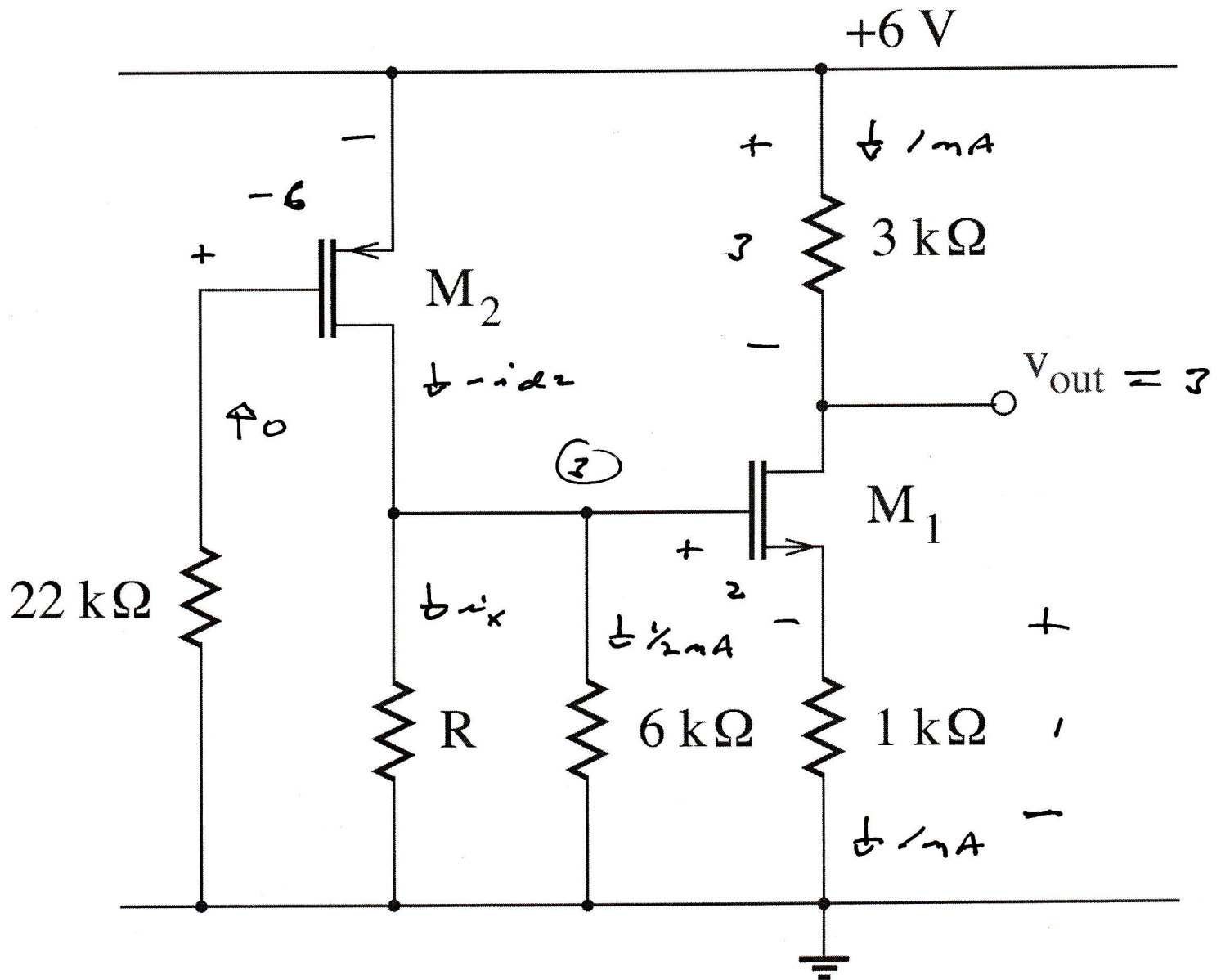
$$M_1 : v_{ds} = 1 = \frac{1}{2} (2) (V_{GS} - 1)^2 \rightarrow V_{GS} = 2, \quad \text{X}$$



$$M_2 \text{ has } v_{ds} = -3, \quad V_{GS} = -6$$

$$-3 > V_{GS} - V_T = -5 \rightarrow \text{resistive mode}$$

$$-v_{ds} = \frac{1}{2} (0.25) [2(-6+1)(-3) - (-3)^2] = 2.625 \text{ mA} \rightarrow i_x = 2.125 \text{ mA}$$


$$R = \frac{3}{2.125} = 1.41 \text{ k}$$

5.48

$$K_n' = 50 \mu\text{A}/\text{V}^2$$

$$n_1: 1 = \frac{1}{2} K_n' \left(\frac{W}{L}\right)_1 (1.5 - 0.5)^2 \rightarrow K_n' \left(\frac{W}{L}\right)_1 = 2 \text{ mA}/\text{V}^2$$
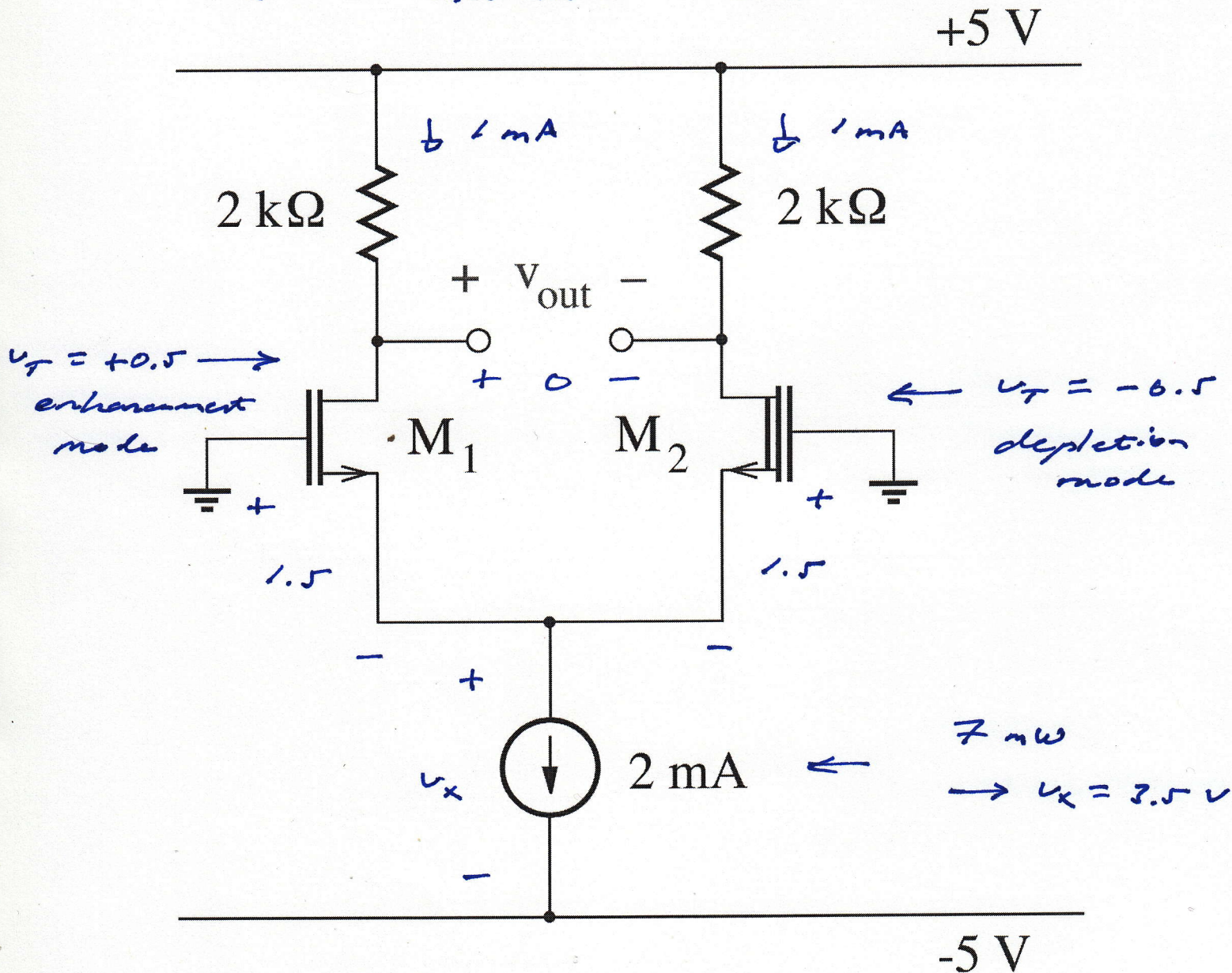
$$\left(\frac{W}{L}\right)_1 = \frac{2 \text{ mA}/\text{V}^2}{0.05 \text{ mA}/\text{V}^2} = \underline{40} \quad V_{ds} = 4.5 > 1.5 - 0.5 \checkmark$$



$$n_2: 1 = \frac{1}{2} K_n' \left(\frac{W}{L}\right)_2 (1.5 + 0.5)^2 \rightarrow K_n' \left(\frac{W}{L}\right)_2 = 0.5 \text{ mA}/\text{V}^2$$

$$\left(\frac{W}{L}\right)_2 = \frac{0.5 \text{ mA}/\text{V}^2}{0.05 \text{ mA}/\text{V}^2} = \underline{10}$$

$$4.5 > 1.5 + 0.5 \checkmark$$