

7.60


$$R_F = R_O = 100$$

$$g_{m1} = \frac{2.2 \text{ mA}}{25.9 \text{ mV}} = 84.9 \times 10^{-3} \text{ S}$$

$$r_{\pi 1} = \frac{\beta_0}{g_{m1}} = 1.18 \text{ k}$$

$$g_{m2} = \frac{1.2 \text{ mA}}{25.9 \text{ mV}} = 46.3 \times 10^{-3} \text{ S}$$

$$r_{\pi 2} = \frac{\beta_0}{g_{m2}} = 2.16 \text{ k}$$

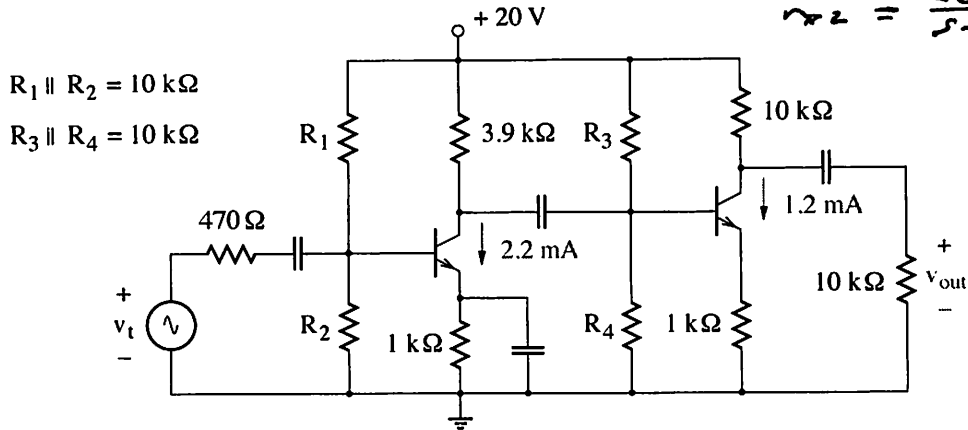

stage 1

stage 2

CE

CE

$$A_{um}^{(2)} = \frac{-g_{m2} r_{ci}}{1 + g_{m2} r_{ci} (1 + \frac{1}{\beta_0})} = -4.85$$

$\uparrow$ 1k

$$r_{in}^{(2)} = R_3 \parallel R_4 \parallel [r_{\pi 2} + (1 + \beta_0) r_{ci}] = 9.12 \text{ k}$$

$\uparrow$ 103k

$$A_{um}^{(1)} = -g_{m1} r_{ci}' = -232$$

$\uparrow$ 3.9k // $r_{in}^{(2)} = 2.73 \text{ k}$

$$r_{in}^{(1)} = R_1 \parallel R_2 \parallel r_{\pi 1} = 1.06 \text{ k}$$

$$LF = \frac{r_{in}^{(1)}}{r_{in}^{(1)} + R_F} = \frac{1.06}{1.06 + 0.47} = 0.693$$

$$A_{um}^{total} = LF \times A_{um}^{(1)} \times A_{um}^{(2)} = \underline{\underline{780}}$$

7.61

$$\beta_F = \beta_0 = 100$$

$$k' \frac{W}{L} = 4.2 \text{ mA/V}^2, V_T = 0.6 \text{ V}$$

$$g_{m1} = \sqrt{2 \times 4.2 \frac{\text{mA}}{\text{V}^2} \times 6 \text{ mA}} = 7.10 \times 10^{-3} \text{ S}$$


$$g_{m2} = \frac{2.5 \text{ mA}}{27.9 \text{ mV}} = 96.5 \times 10^{-3} \text{ S}$$

$$r_{o2} = \frac{\beta_0}{g_{m2}} = 1.04 \text{ k}\Omega$$

$$A_{vm}^{(2)} = g_{m2} r_{o2}' = 96.5 \times 10^{-3} \text{ S} \times 3.20 \times 10^3 \Omega = 309$$

$$R_1 \parallel R_2 = 100 \text{ k}\Omega$$
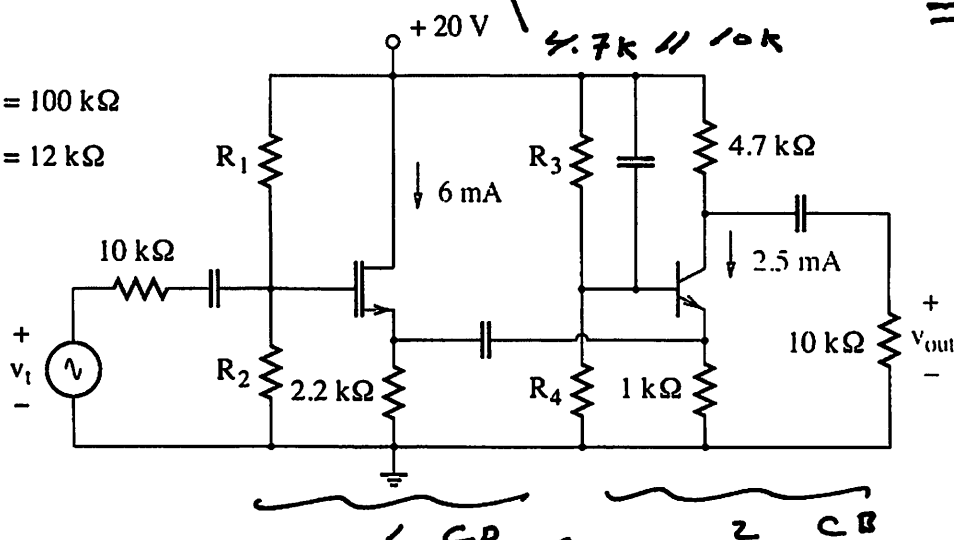
$$R_3 \parallel R_4 = 12 \text{ k}\Omega$$



$$r_{in}^{(2)} = 1 \text{ k}\Omega \parallel \frac{r_{\pi 2}}{1 + \beta_0} = 10.2 \Omega$$

$$A_{vm}^{(1)} = \frac{g_{m1} r_{in}^{(2)}}{1 + g_{m1} r_{in}^{(2)}} = \frac{0.0724}{1 + 0.0724} = 0.0675$$

$$r_{in}^{(1)} = R_1 \parallel R_2 = 100 \text{ k}\Omega$$

$$L_F = \frac{r_{in}^{(1)}}{r_{in}^{(1)} + r_{in}^{(2)}} = \frac{100 \text{ k}\Omega}{100 \text{ k}\Omega + 10 \text{ k}\Omega} = 0.909$$

$$A_{vm}^{TOTAL} = 0.909 \times 309 = 190$$

7.62

$$K' \frac{W}{L} = 2.2 \text{ mA/V}^2$$


$$g_{m1} = \sqrt{2 \mu_n C_{ox} K' \frac{W}{L}} = 2.10 \times 10^{-3} \text{ V}$$

$$r_{o1} = \infty$$

$$\beta_0 = 120$$

$$g_{m2} = \frac{v_{GS2}}{kT/q} = \frac{0.1 \text{ mA}}{25.8 \text{ mV}} = 3.86 \times 10^{-3} \text{ V}$$

$$r_{o2} = \frac{\beta_0}{g_{m2}} = 31.1 \text{ k}$$

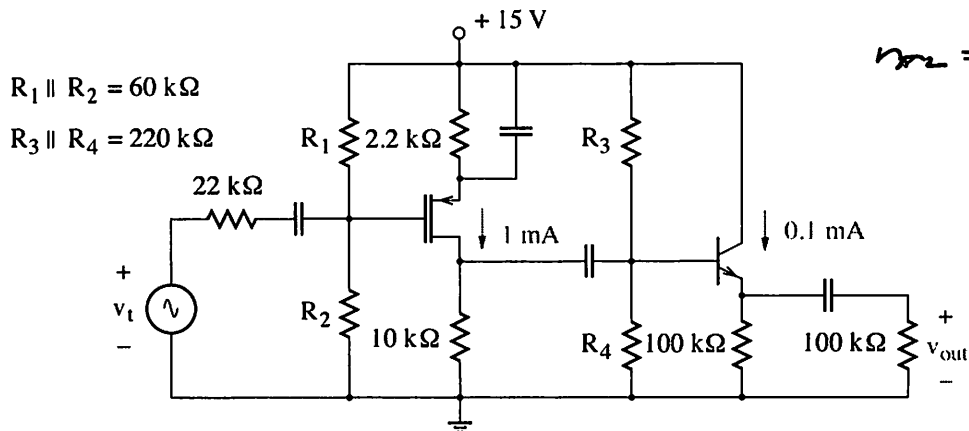

stage 1

stage 2

C.S. 100k // 100k C.C.

$$A_{vm}^{(2)} = \frac{g_{m2} r_{e2}' (1 + \frac{1}{\beta_0})}{g_{m2} r_{e2}' (1 + \frac{1}{\beta_0}) + 1} = \frac{195}{195 + 1} = 0.995$$

$$r_{in}^{(2)} = r_3 // r_4 // [r_{o2} + (\beta_0 + 1) r_{e2}'] = \cancel{212 \text{ k}} \quad \begin{matrix} \uparrow \\ 6.08 \text{ M}\Omega \end{matrix} \quad \begin{matrix} \uparrow \\ 50 \text{ k} \end{matrix}$$

$$A_{vm}^{(1)} = -g_{m1} r_{e1}' = \cancel{-20.0} \quad \begin{matrix} \uparrow \\ 10 \text{ k} // r_{in}^{(2)} = \cancel{8.5 \text{ k}} \end{matrix}$$

$$r_{in}^{(1)} = r_1 // r_2 = 60 \text{ k}$$

$$LF = \frac{r_{in}^{(1)}}{r_{in}^{(1)} + R_t} = \frac{60}{60 + 22} = 0.732$$

$$A_{vm}^{total} = LF \times A_{vm}^{(1)} \times A_{vm}^{(2)} = \cancel{-15}$$

$$7.63 \quad \beta_F = \beta_0 = 140$$

$$K' \frac{W}{L} = 1.8 \text{ mA/V}^2, \quad V_T = 0.7 \text{ V}$$


$$g_{m1} = \sqrt{2 \times 1.8 \text{ mA/V}^2 \times 0.5 \text{ mA}} = 1.34 \times 10^{-3} \text{ S}$$

$$g_{m2} = \frac{3 \text{ mA}}{25.9 \text{ mV}} = 116 \times 10^{-3} \text{ S}$$

$$r_{\pi 2} = \frac{\beta_0}{g_{m2}} = 1.21 \text{ k}\Omega$$

$$A_{vm}^{(2)} = \frac{-g_{m2} R_{c2}'}{1 + g_{m2} R_{e2}' (1 + \frac{1}{\beta_0})}$$
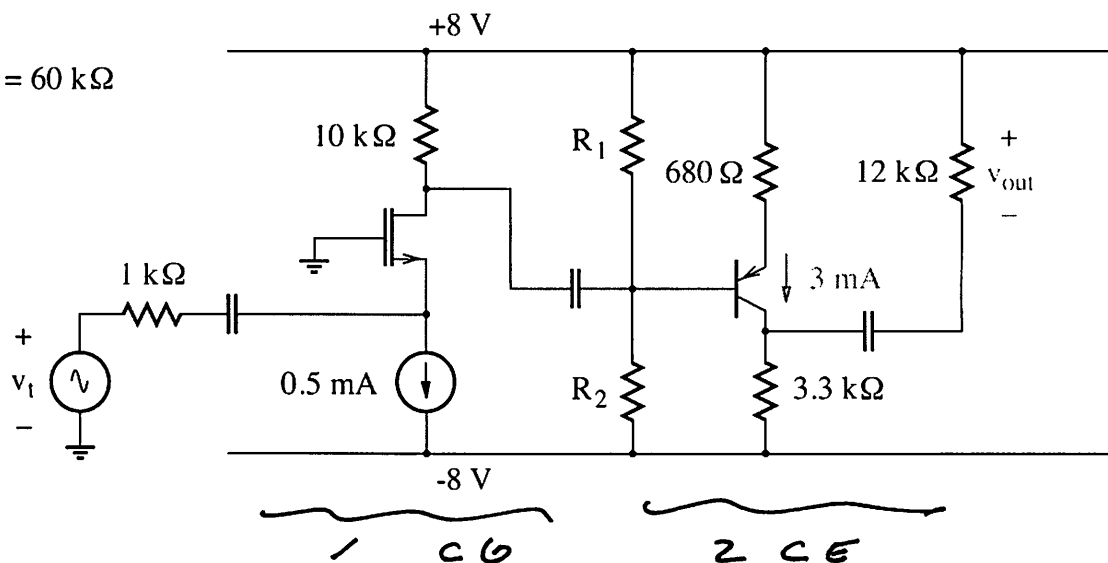
$$R_1 \parallel R_2 = 60 \text{ k}\Omega$$



$$R_{c2}' = 3.3 \text{ k}\Omega \parallel 12 \text{ k}\Omega = 2.59 \text{ k}\Omega$$

$$R_{e2}' = 680 \Omega$$

$$A_{vm}^{(2)} = \frac{-116 \times 10^{-3} \text{ S} \times 2.59 \times 10^3 \Omega}{1 + 116 \times 10^{-3} \text{ S} \times 0.68 \times 10^3 \Omega (1 + \frac{1}{140})}$$

$$= -3.74$$

$$r_{in}^{(2)} = (r_{i1} || r_{i2}) || \underbrace{[r_{i2} + (1 + \beta_0) r_{e2}']}_{60K}$$

$$\rightarrow 1.21K + 141 \times 0.68K = 97.1K$$

$$= 37.1K$$

$$A_{vm}^{(1)} = g_{m1} r_{di}'$$

$$\uparrow 10K || r_{in}^{(2)} = 7.88K$$

$$= 1.24 \times 10^{-3} V \times 7.88 \times 10^3 \Omega = 10.6$$

$$r_{in}^{(1)} = \frac{1}{g_{m1}} = 746 \Omega$$

$$LF = \frac{r_{in}^{(3)}}{r_{in}^{(2)} + r_{in}^{(1)}} = \frac{0.746}{0.746 + 1} = 0.427$$

$$A_{vm}^{TOTAL} = 0.427 \times 10.6 \times (-3.74)$$

$$= \underline{\underline{-16.9}}$$