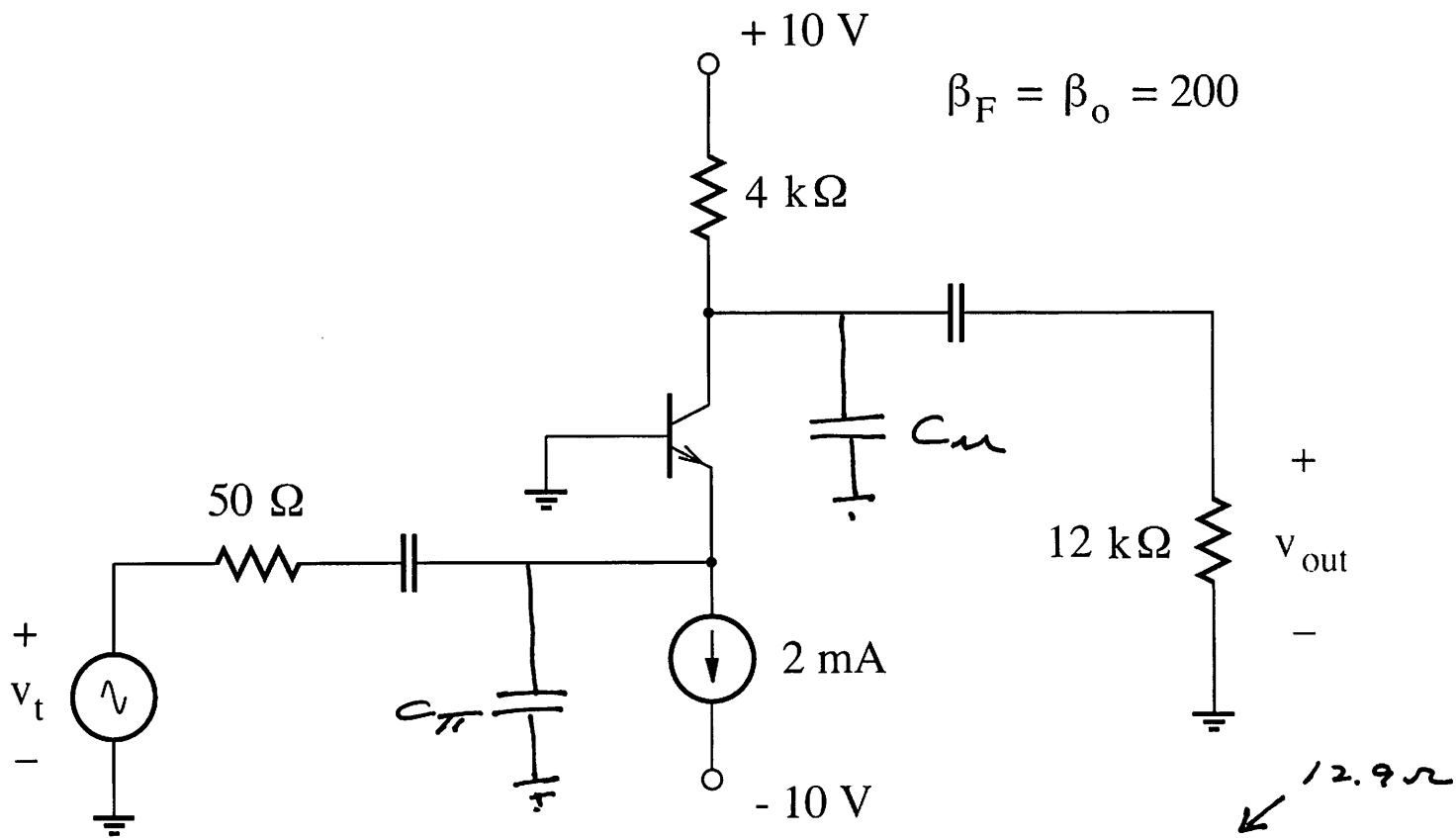


~~8.12~~  
8.12

$$C_{\pi} = 2.5 \text{ pF}, C_{\mu} = 1.5 \text{ pF}$$

$$g_m = \frac{2 \text{ mA}}{25.9 \text{ mV}} = 77.2 \times 10^{-3} \text{ S}$$

$$\tau_1(C_{\mu}) : \tau_1 = 1.5 \times 10^{-12} \times \underbrace{(4 \text{ k}\Omega // 12 \text{ k}\Omega)}_{3 \times 10^3} = 4.5 \text{ ns}$$



$$\tau_2(C_{\pi}) : \tau_2 = 2.5 \times 10^{-12} \times \left( 50 \Omega // \frac{1}{g_m(1 + \frac{1}{\beta_0})} \right)$$

$\frac{1}{10.2 \text{ S}}$

$$= 0.026 \text{ ns}$$

$$\Sigma \tau = 4.526 \text{ ns}$$


$$f_h \approx \frac{1}{2\pi \Sigma \tau} = \underline{\underline{35.2 \text{ MHz}}}$$

8.17

$$C_{gs} = 2.5 \text{ pF}, \quad C_{gd} = 1.5 \text{ pF}$$

$$A_{vm} = -6 \quad (\text{see Exercise 7.10})$$
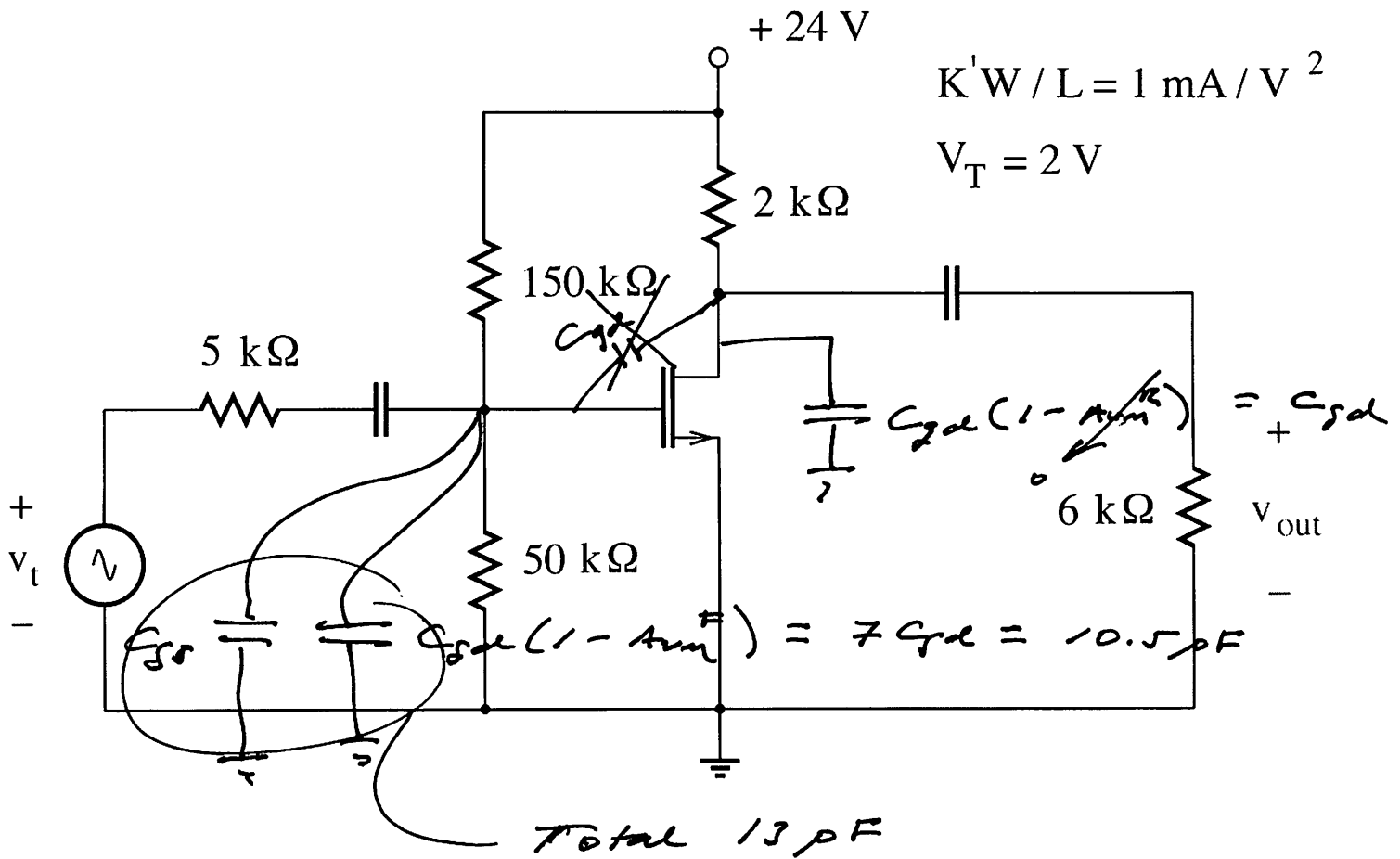
$$\tau_{\text{output}} = 1.5 \times 10^{-12} \times \frac{(2 \text{ k} \parallel 6 \text{ k})}{1.5 \text{ k}} = 2.25 \text{ ns}$$




$$\tau_{\text{input}} = 13 \times 10^{-12} \times \frac{(5 \text{ k} \parallel 50 \text{ k} \parallel 150 \text{ k})}{4.41 \text{ k}} = 57.3 \text{ ns}$$

$$\Sigma \tau = 59.6 \text{ ns}$$


$$f_h \approx \frac{1}{2\pi \Sigma \tau} = 2.67 \text{ MHz}$$

8.24

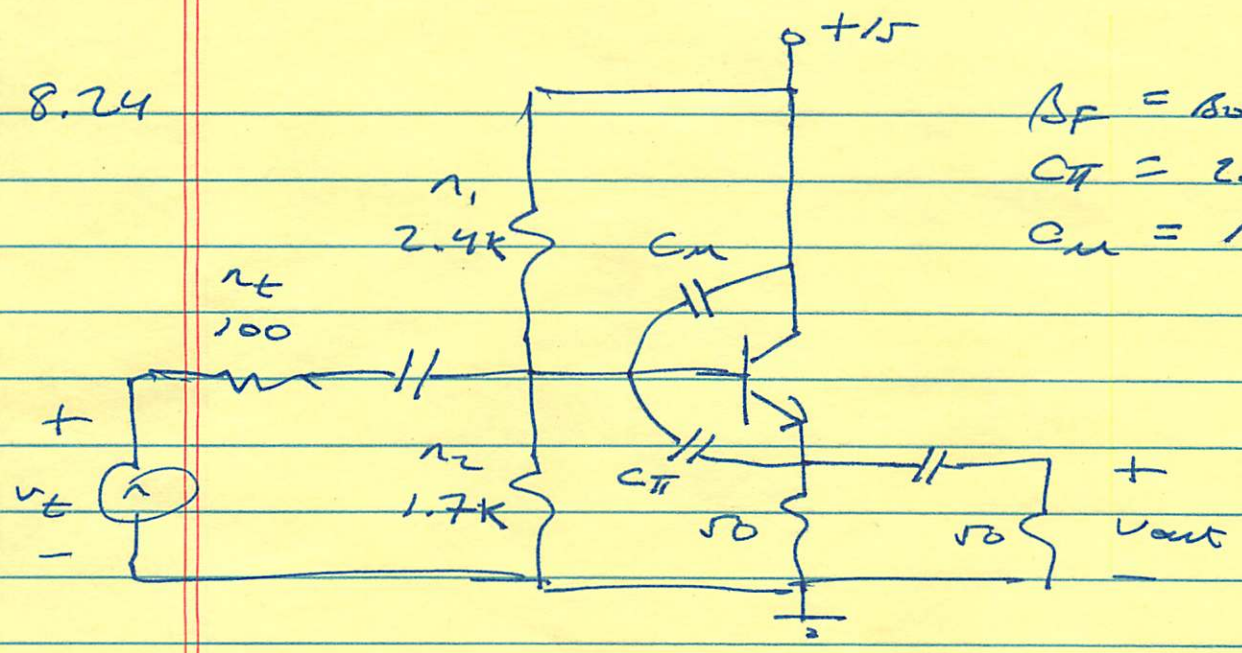

$\beta_F = \beta_0 = 200$   
 $C_{\pi} = 2.5 \text{ pF}$   
 $C_{\mu} = 1.5 \text{ pF}$

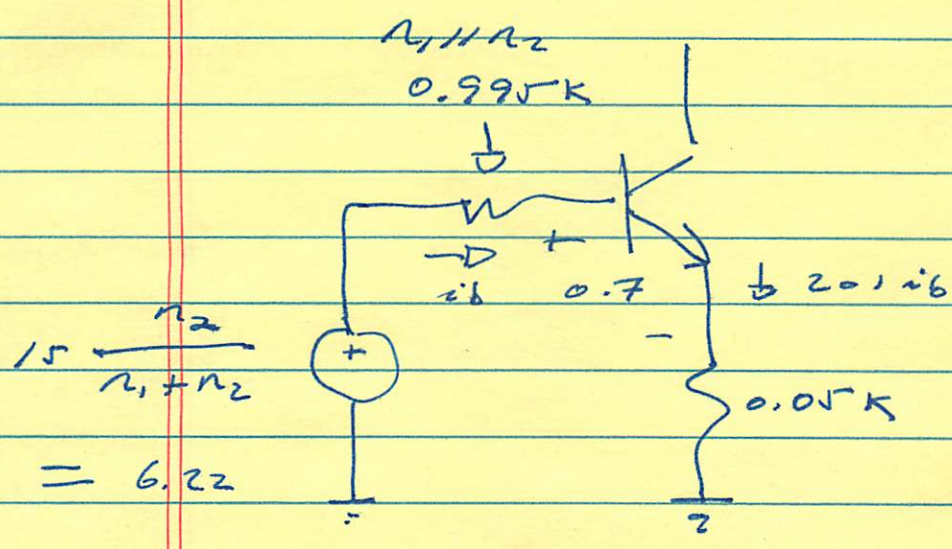Need the Q point for  $g_m, r_{\pi}, A_{v_m}$ , etc.



$$\frac{15 \cdot n_2}{n_1 + n_2} = 6.22$$

$$6.22 = 0.995 i_b + 0.7 + 201(0.05) i_b$$

$$i_b = \frac{5.52}{11.0}$$

$$i_{c1Q} = \frac{5.52}{11} (200) = 100 \text{ mA}$$


$$V_{ce1Q} = 15 - (100)(0.05) = 10 \text{ V}$$

✓ forward active

$$g_m = \frac{i_{c1Q}}{kT/q} = \frac{100 \text{ mA}}{25.9 \text{ mV}} = 3.86 \text{ V}^{-1}$$

$$r_{\pi} = \beta_0 / g_m = 200 / 3.86 = 51.8 \Omega$$

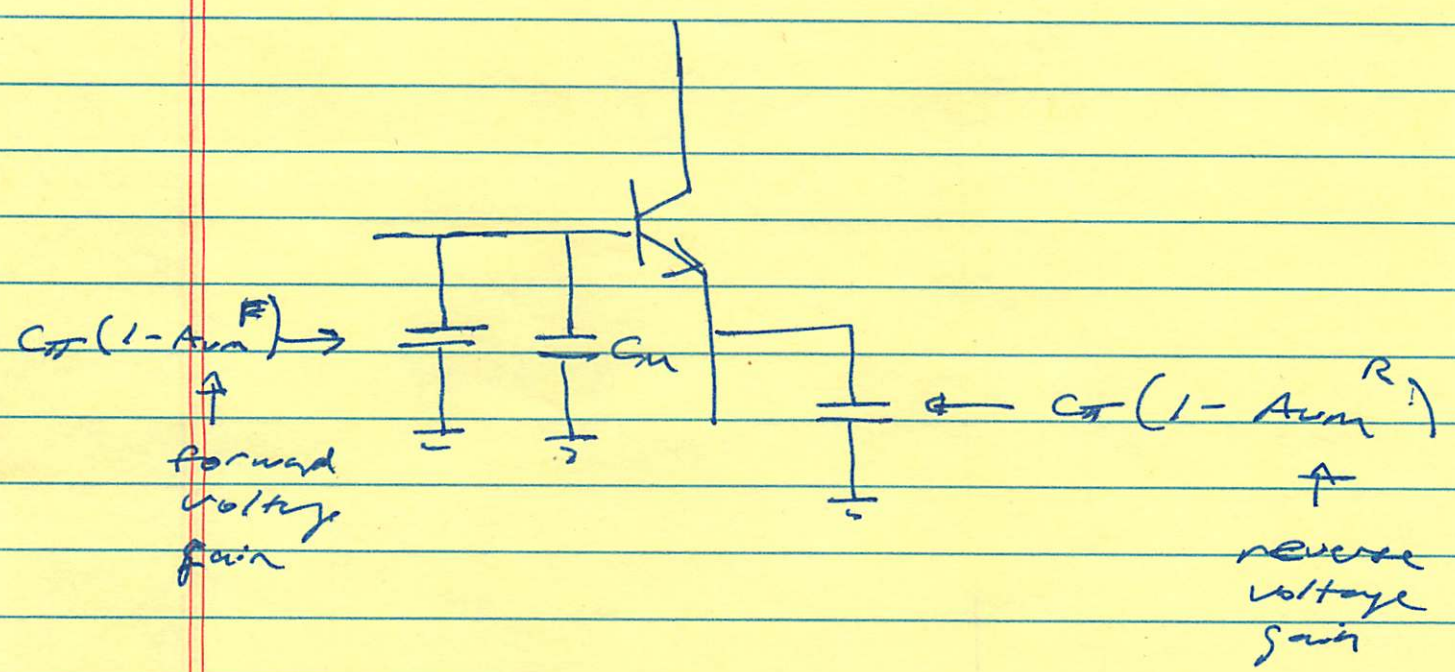$C_{\mu}$  connects from base to ac  $\frac{1}{s}$   
 $C_{\mu}$  is a feedback cap.  $\rightarrow$  Miller time



$$A_{vV}^F \text{ (common collector)} = \frac{g_m R_e' (1 + 1/\beta_0)}{1 + g_m R_e' (1 + 1/\beta_0)}$$

$$R_e' = 50\Omega // 50\Omega = 25\Omega$$


(looking away from emitter)

$$\rightarrow A_{vV}^F = 0.990$$

$$C_{\mu}(1 - A_{vV}^F) = 0.025 \text{ pF} \quad \text{small}$$

$$C_{\mu} + C_{\mu}(1 - A_{vV}^F) = 1.525 \text{ pF}$$

$A_{um}^n$

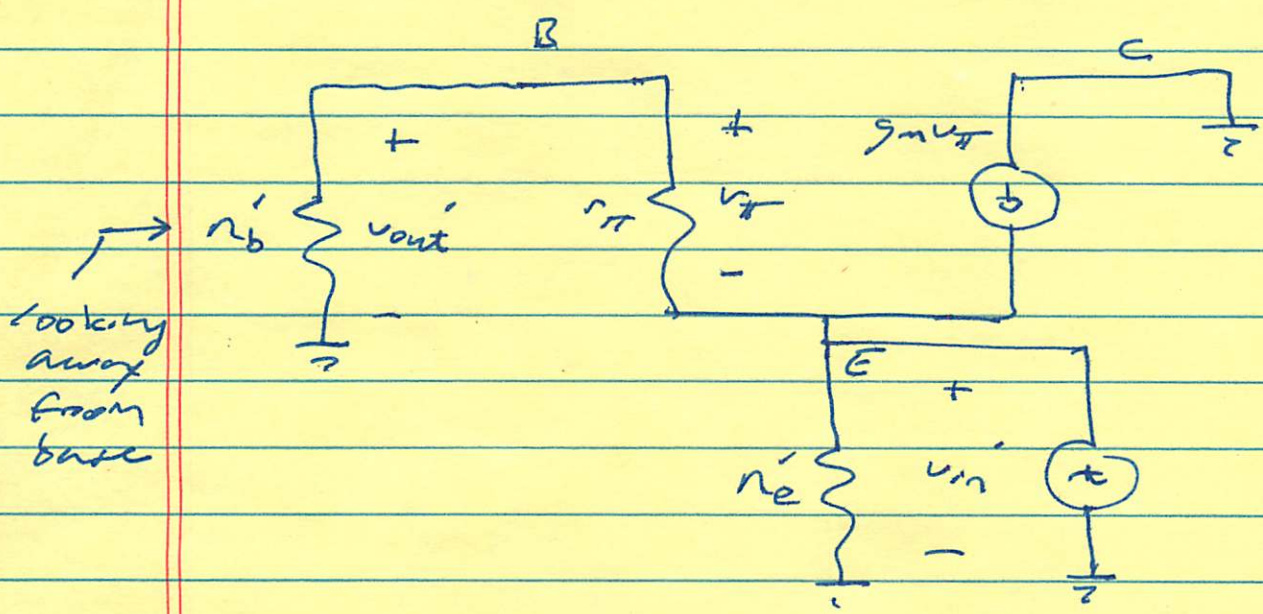

$$\frac{v_{out}'}{v_{in}'} = A_{um}^n = \frac{r_b'}{r_{\pi} + r_b'}$$

(This situation - BJT, feedback from emitter, is the only  $A_{um}^n \neq 0$ .)

$$r_b' = r_1 \parallel r_2 \parallel r_e = 90.9 \Omega$$

$$\rightarrow A_{um}^n = \frac{90.9}{51.8 + 90.9} = 0.637$$

$$C_{\pi} (1 - A_{um}^n) = 0.908 \text{ pF}$$

$$r_1 = \text{resistance to } \frac{1}{2} \text{ "seen" by } C_{in} + C_{\pi} [1 - A_{mid}^2]$$

$$= \underbrace{r_{\pi} \parallel r_2 \parallel R_E}_{90.9 \Omega} \parallel r_b'$$

↑  
resistance looking into base

$$r_b' = r_{\pi} + (1 + \beta_0) r_e' = 5.08 \text{ k}$$

↑ 200 Ω ← Table 8.1

↳  $r_1 \approx 89.3 \Omega$

$$\tau_1 = 1.525 \times 10^{-12} \times 89.3 = 0.136 \text{ ns}$$

$$r_2 = \text{resistance to } \frac{1}{2} \text{ "seen" by } C_{\pi} [1 - A_{mid}^2]$$

$$= 50 \parallel 50 \parallel r_e'$$

↑  
resistance looking into emitter

$$r_e' = \frac{r_{\pi} + r_b'}{1 + \beta_0} \quad \leftarrow \text{see Table 8.1}$$

$$= \frac{51.8 \Omega + 90.9 \Omega}{201} = 0.71 \Omega$$

↳  $r_2 = 0.69 \Omega$

$$\tau_2 = 0.908 \times 10^{-12} \times 0.69 = 0.62 \text{ ps}$$

negligible

$$f_T \approx \frac{1}{2\pi \tau_T} = \underline{1.2 \text{ GHz}}$$


8.33

$$k' \frac{W}{L} = 2 \text{ mA/V}^2 \quad V_T = 0.7 \text{ V}$$


$$C_{gs} = 0.2 \text{ pF}, \quad C_{gd} = 0.1 \text{ pF}$$

$$C_{db} = C_{sb} = 0.2 \text{ pF} \quad (\text{body cap.})$$
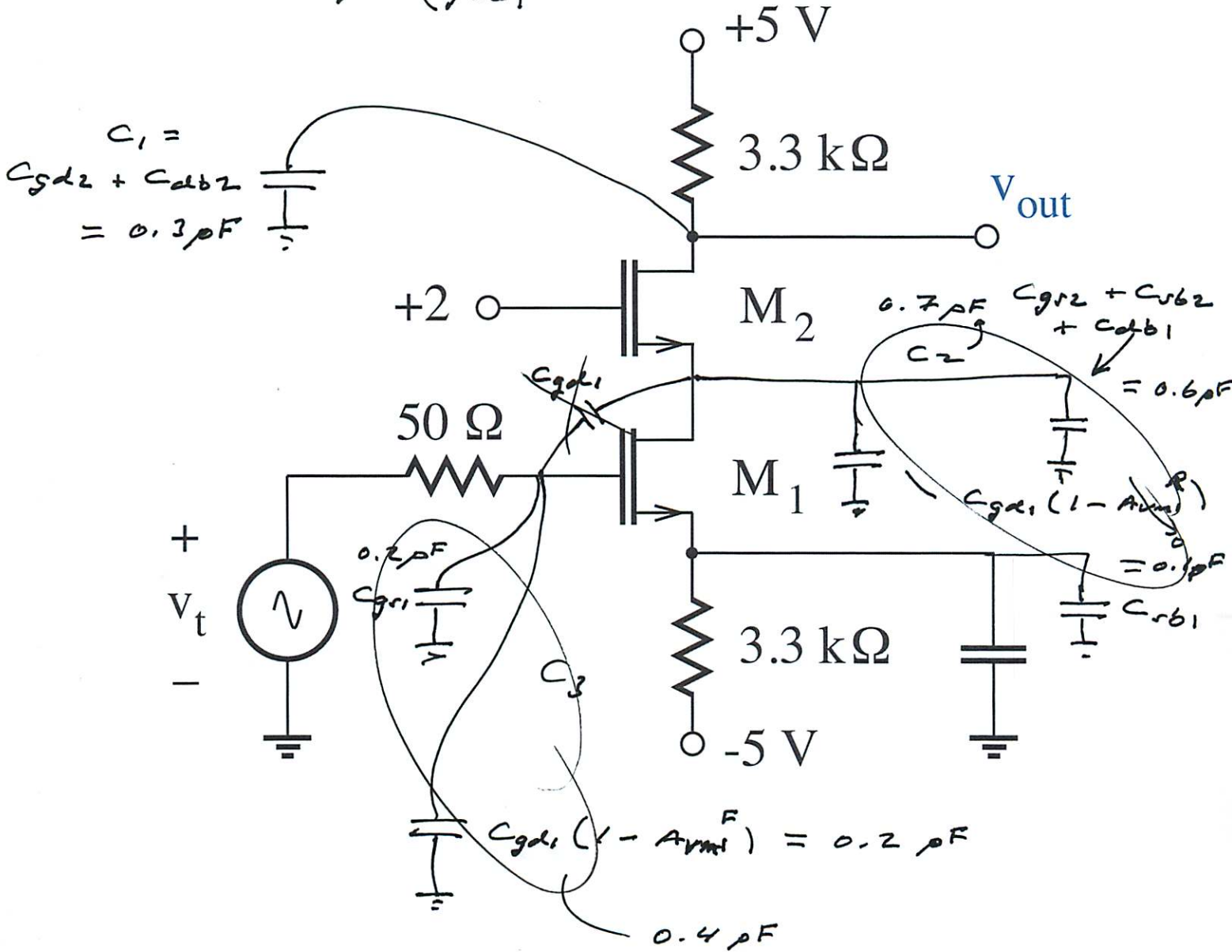
$$A_{vm1}^F = -g_{m1} \left( \frac{1}{g_{m2}} \right) = -1 \quad \leftarrow \text{same size } M_1, M_2$$



## m. biasing

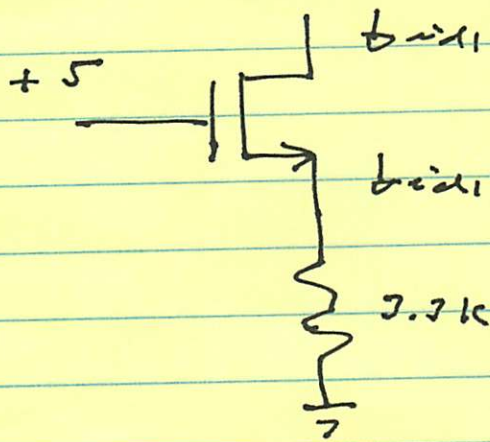

$$V_{GS} = 5 - 3.3 i_{d1}$$

$$i_{d1} = \frac{1}{2} (2) (V_{GS} - 0.7)^2$$

$$V_{GS} = 5 - 3.3 V_{GS}^2 + 4.62 V_{GS} - 1.62$$

$$3.3 V_{GS}^2 - 3.62 V_{GS} - 3.38 = 0$$

$$V_{GS} = \frac{3.62 \pm \sqrt{13.1 + 44.6}}{6.6}$$

$$= 1.7 \text{ V}, -0.6 \text{ V}$$

$$i_{d1} = \frac{1}{2} (2) (1.7 - 0.7)^2 = 1 \text{ mA}$$
$$= i_{d2} = i_Q$$

$$g_{m1} = g_{m2} = g_m = \sqrt{2 \times 2 \text{ mA/V}^2 \times 1 \text{ mA}}$$

$$= 2 \times 10^{-3} \text{ S}$$



$$m_2 \text{ drain: } C_1 = 0.3 \text{ pF}$$

$$\tau_1 = 0.2 \text{ pF} \times 2.5 \text{ k} = 0.99 \text{ ns}$$

$$m_2 \text{ source: } C_2 = 0.7 \text{ pF}$$

$$r_{eq}^{(2)} = \frac{1}{g_{m2}} = 0.5 \text{ k}$$

$$\tau_2 = 0.7 \text{ pF} \times 0.5 \text{ k} = 0.35 \text{ ns}$$

$$m_1 \text{ gate: } C_3 = 0.4 \text{ pF}$$

$$r_{eq}^{(3)} = 50 \Omega$$

$$\tau_3 = 0.4 \text{ pF} \times 0.05 \text{ k} = 0.02 \text{ ns}$$

$$\sum \tau = 1.36 \text{ ns}$$

$$f_h \approx \frac{1}{2\pi \sum \tau} = 11.7 \text{ MHz}$$