


9.4

$$\beta_D = 100$$

$$i_X = \frac{10 - 0.7}{20k} =$$

$$0.465 \text{ mA}$$

Q-point analysis:

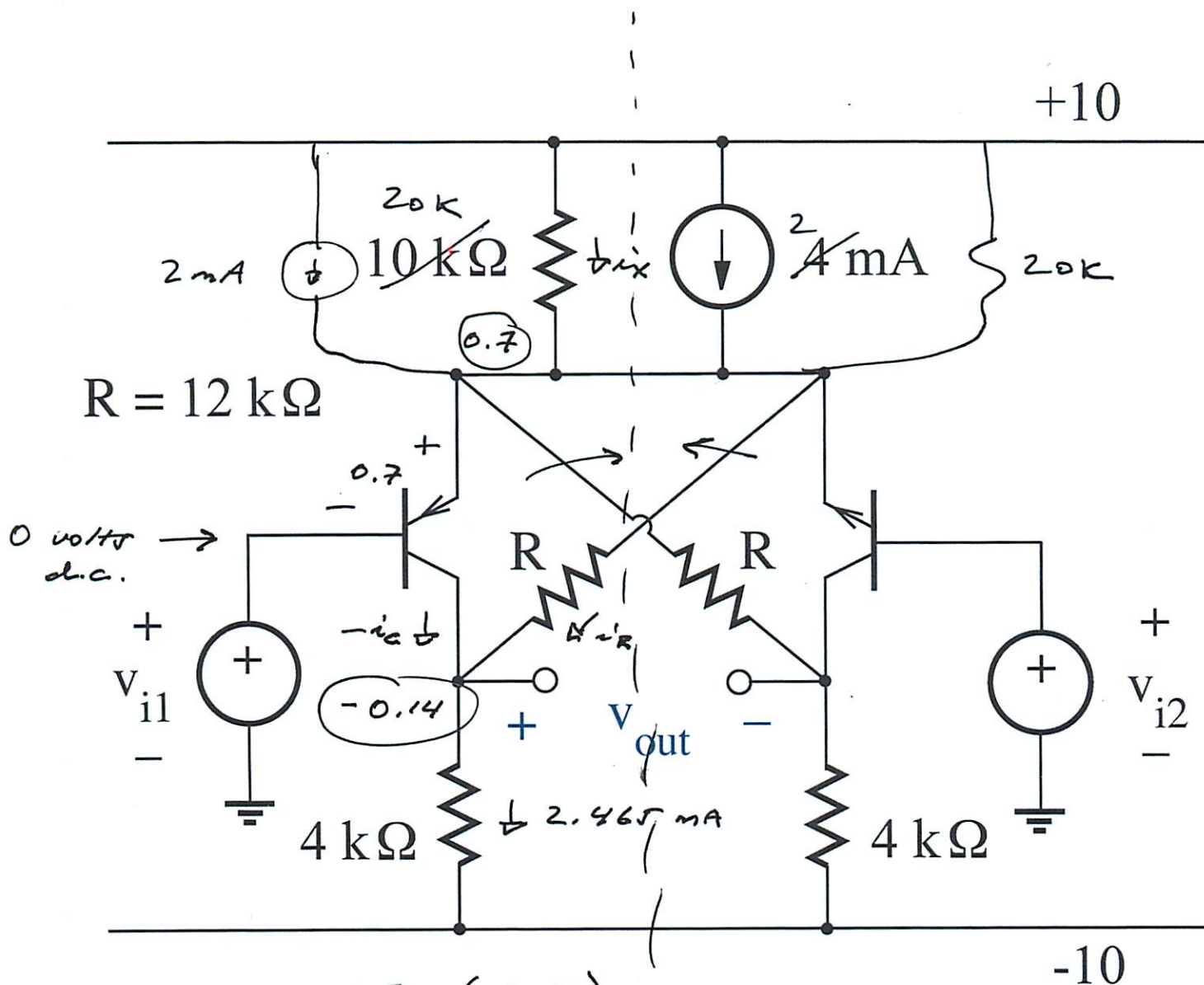


$$i_R = \frac{0.7 - (-0.14)}{12k} = 0.07 \text{ mA}$$

$$\rightarrow -i_c = 2.465 \text{ mA} - 0.07 \text{ mA} \approx 2.40 \text{ mA}$$

$$\rightarrow f_m = \frac{2.40 \text{ mA}}{25.9 \text{ mV}} = 92.7 \times 10^{-3} \text{ V}$$

A_{ddl}
1/2 ckt.

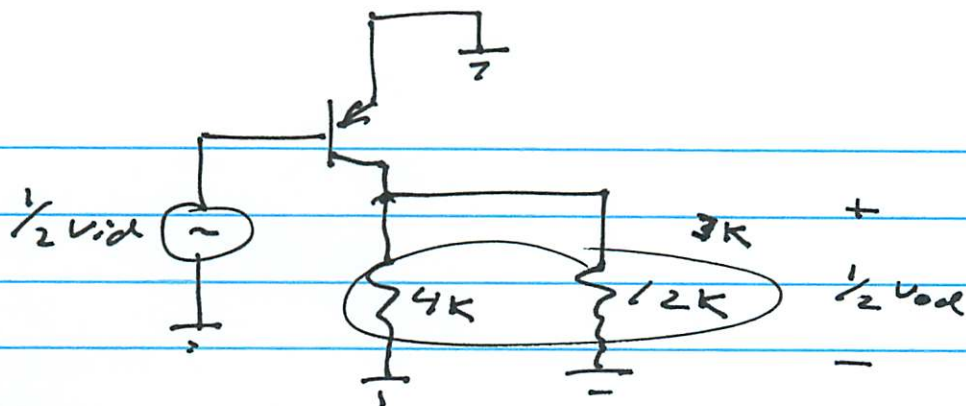


$$\frac{\frac{1}{2} v_{od}}{\frac{1}{2} v_{id}} = A_{ddl} = -g_m (3k)$$

$$= -92.7 \times 10^{-3} \text{ V} \times 3 \times 10^3 \Omega$$

$$= -278$$

A_{cc}
1/2 ckt.

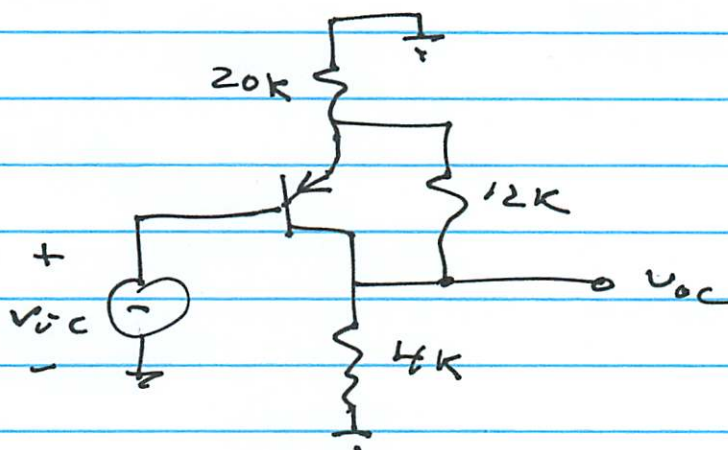

$$R_{c'} = 4k$$

$$R_{e'} = 20k$$

Table 9.2

$$r_o \rightarrow 12k$$



$$\frac{v_{oc}}{v_{ic}} = A_{cc} = \frac{-g_m (R_{c'} // r_o)}{1 + g_m R_{e'} (1 + \frac{1}{\beta}) / (1 + \frac{R_{c'}}{r_o})}$$

$$A_{cc} = \frac{-92.7 \times 10^{-3} \times 3 \times 10^3}{1 + 92.7 \times 10^{-3} \times 20 \times 10^3 \times (1.01) / 1.33}$$

$$= -0.197$$

9.7

$$K' \frac{W}{L} = 2 \text{ mA/V}^2 \quad V_T = -0.5 \text{ V}$$


Q-point analysis:

$$-i_d = \frac{10 + V_{gs}}{20} = 1 (V_{gs} + 0.5)^2$$

$$10 + V_{gs} = 20 V_{gs}^2 + 20 V_{gs} + 5$$

$$20 V_{gs}^2 + 19 V_{gs} - 5 = 0 \quad \xrightarrow{+10} \quad V_{gs} = \frac{-19 \pm \sqrt{19^2 + 400}}{40}$$

$$-1.17 \text{ V}$$

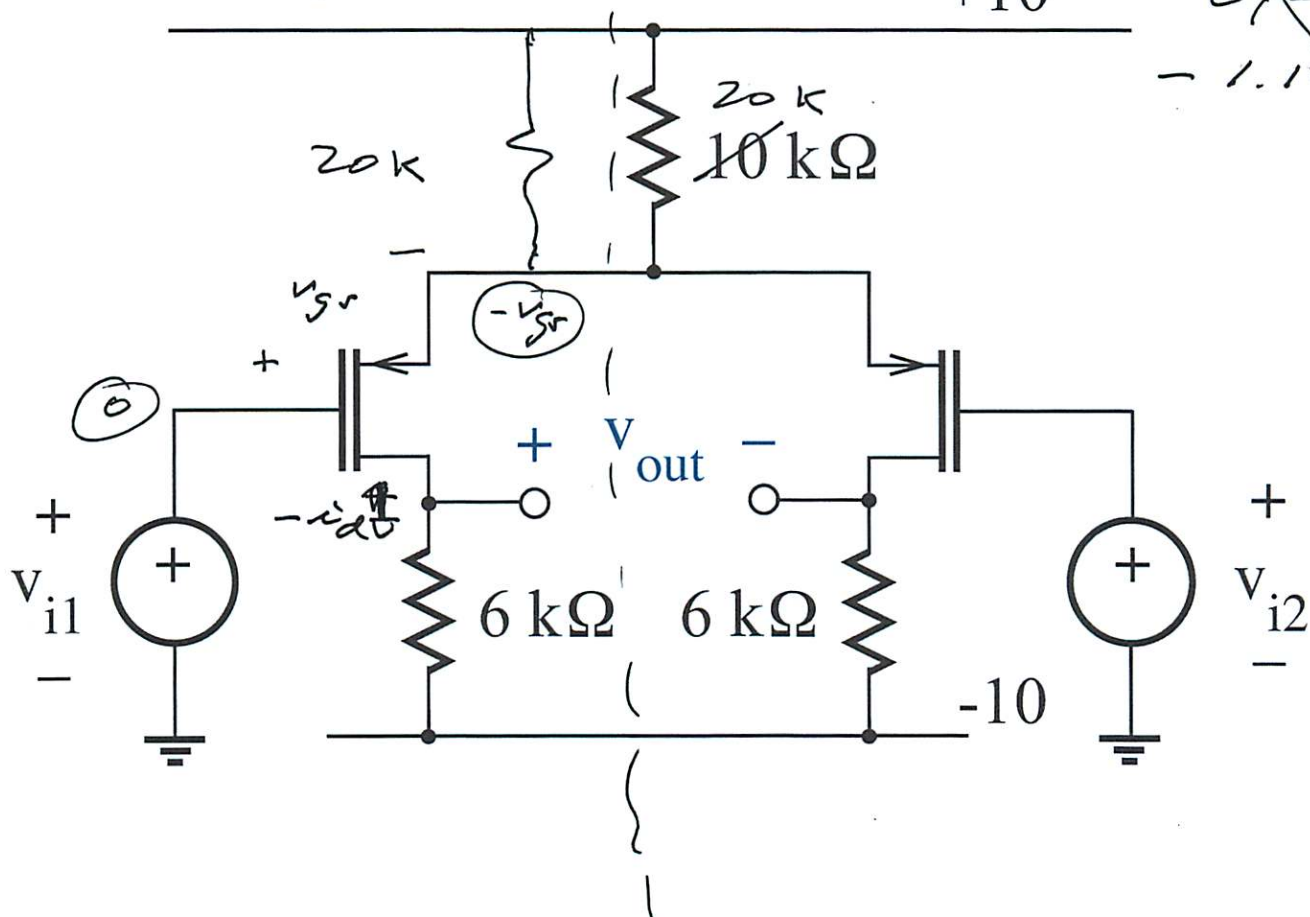


$$-i_{d1Q} = 1 (-1.17 + 0.5)^2 = 0.449 \text{ mA}$$

$$S_m = \sqrt{2 \times 2 \frac{\text{mA}}{\text{V}^2} \times 0.449 \text{ mA}}$$

$$= 1.34 \times 10^{-3} \text{ V}$$


A_{ddl}
 $\frac{1}{2}$ ckt.

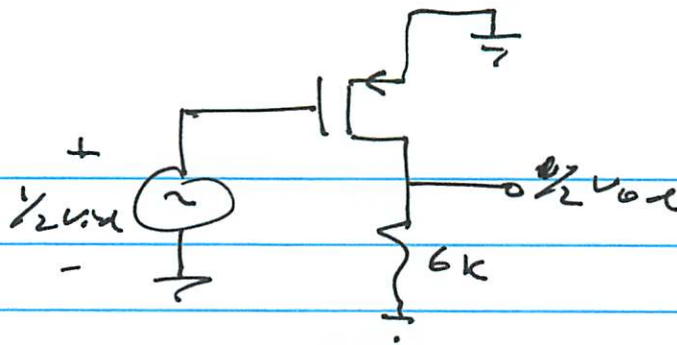

$$\frac{\frac{1}{2} v_{od}}{\frac{1}{2} v_{id}} = A_{ddl} = -g_m(6k)$$

$$= -1.34 \times 10^{-2} \text{ V} \times 6 \times 10^3 \Omega = -8.04$$

A_{cc}
 $\frac{1}{2}$ ckt.

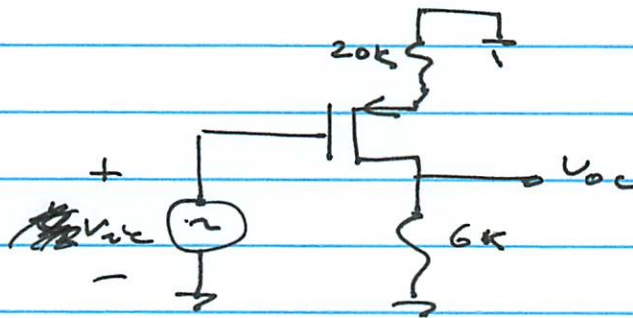


$$A_{cc} = \frac{v_{oc}}{v_{ic}} = \frac{-g_m(6k)}{1 + g_m(20k)}$$

$$= \frac{-8.04}{1 + 1.34 \times 10^{-2} \text{ V} \times 20 \times 10^3 \Omega}$$

$$= -0.289$$

$$CMRR = 20 \log \left(\frac{-8.04}{-0.289} \right) = \underline{\underline{28.9 \text{ dB}}}$$

9.17

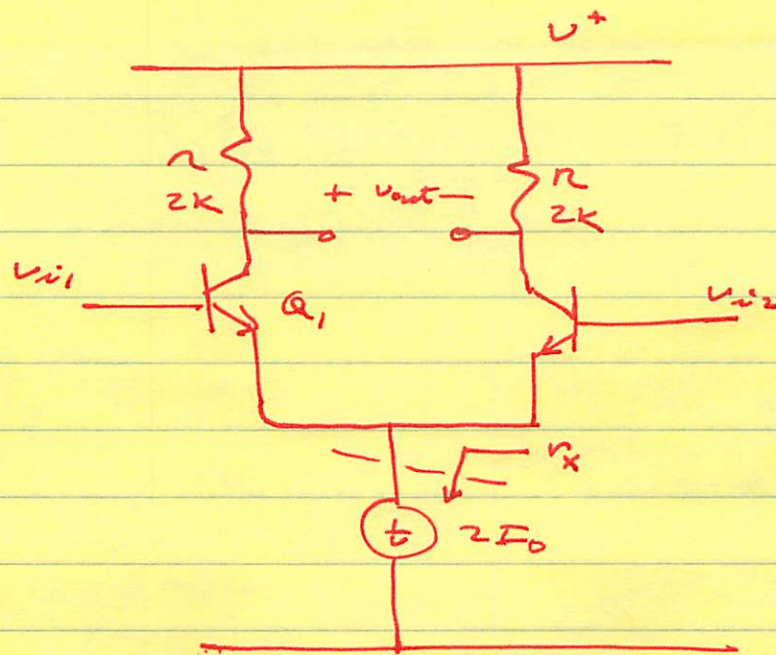

$$\beta_F = 100$$

$$A_{de} = -g_m R = -100 \rightarrow g_m = \frac{100}{2000} = 0.05 \text{ V}$$

$$g_m = \frac{I_0}{kT/2} \rightarrow I_0 = 0.05 \times 0.0259 \text{ V} = 1.3 \text{ mA}$$

$$A_{cc} = \frac{-g_m R}{1 + 2r_x g_m (1 + \frac{1}{\beta_0})} = -0.001$$

↑
should be negative

$$1 + 2r_x g_m (1 + \frac{1}{\beta_0}) = \frac{-100}{-0.001} = 10^5$$

$$r_x \approx \frac{10^5}{2 \times 0.05 \times 1.01} = 990 \text{ k}$$

9.18


A_v before (9.17) ~~before~~ $-g_m R = A_{dd}$

$= -100$

$$g_m = 0.05 \text{ V}$$

$$= \sqrt{2K' \frac{W}{L} i_{d1Q}}$$
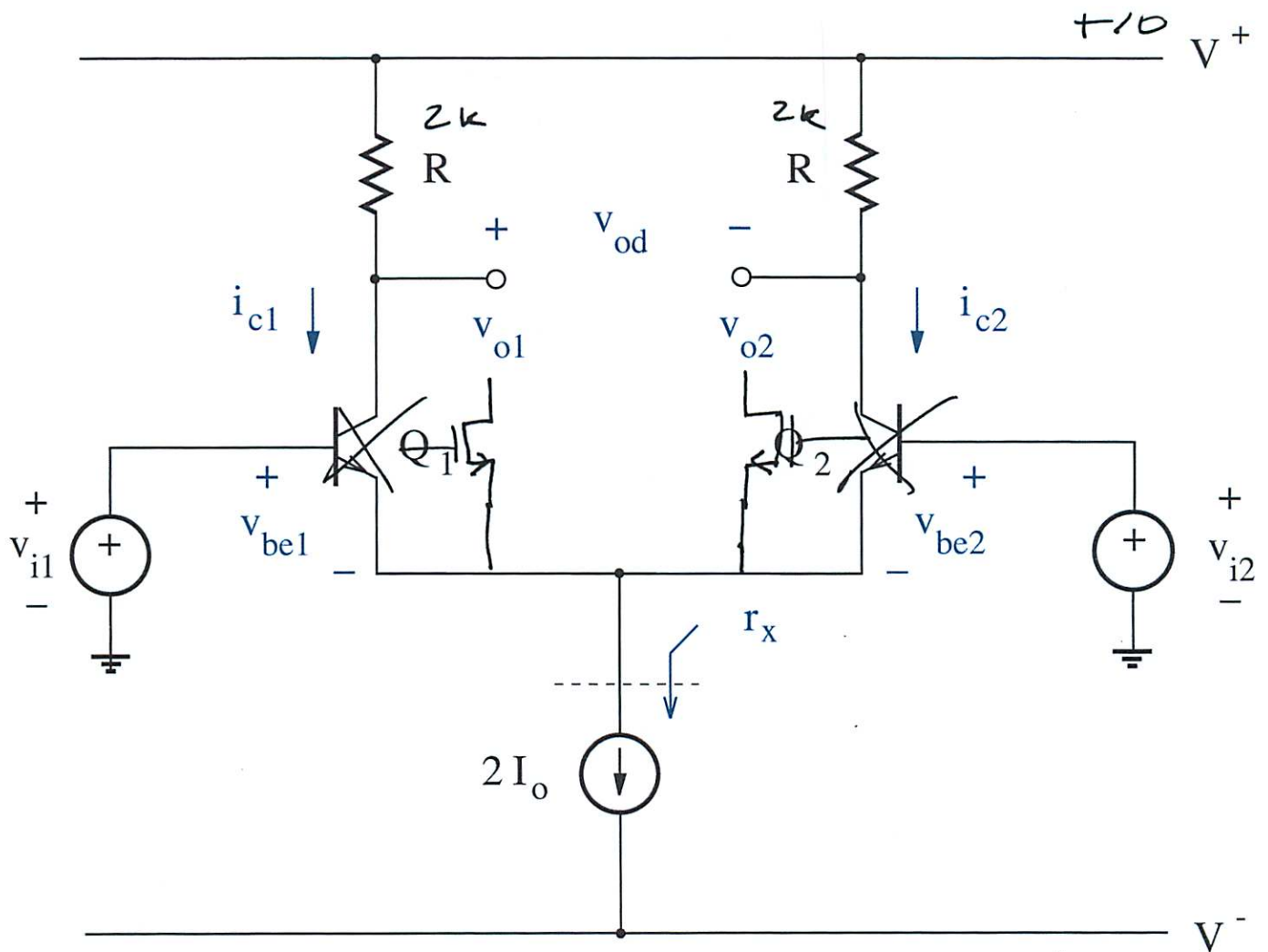
$$\text{Let } i_{d1Q} = I_0 = 1 \text{ mA}$$



$$g_m^2 = 5 \times 10^{-4} = 2 \times 50 \times 10^{-6} \left(\frac{W}{L} \right) \times 10^{-3}$$

$$\Rightarrow \frac{W}{L} = 5000$$

$I_0 = 10 \text{ mA}$
probably better

$$A_{cc} = \frac{-g_m R}{1 + 2g_m r_x}$$

$$\rightarrow r_x \approx 1 \text{ M}\Omega$$

$$K_n' = 50 \mu\text{A/V}^2 \quad V_T = 0.5 \text{ V}$$