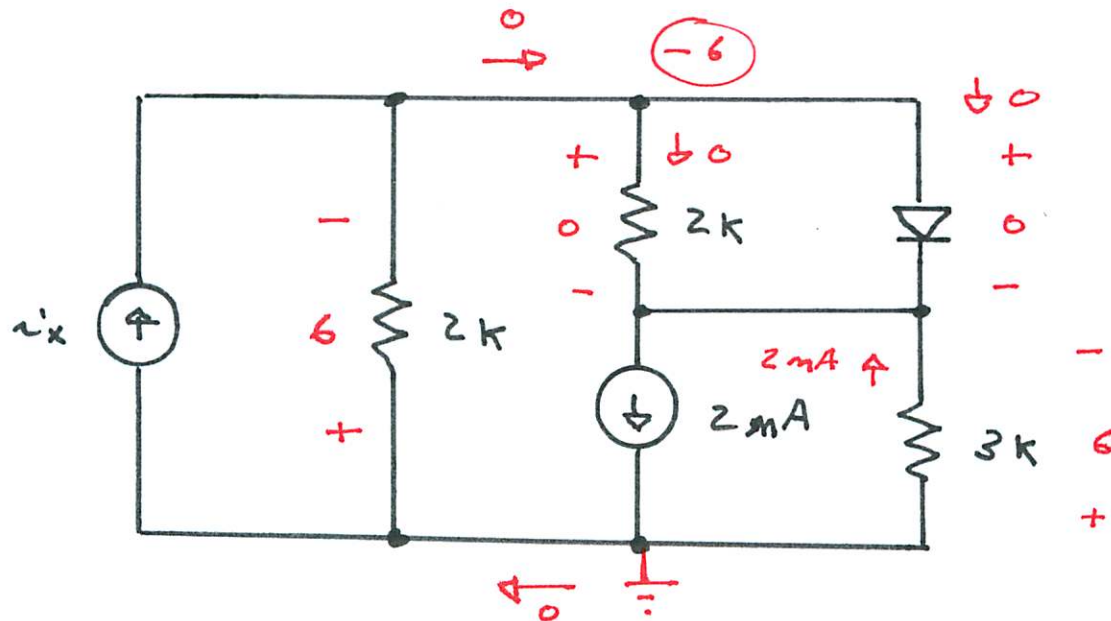


Problem 1

Determine the range of i_x that puts the diode in the "on" state.

The diode is ideal.




diode breakpoint when $i_x = \frac{-6}{2k} = -3mA$

diode "on" for $i_x > -3mA$

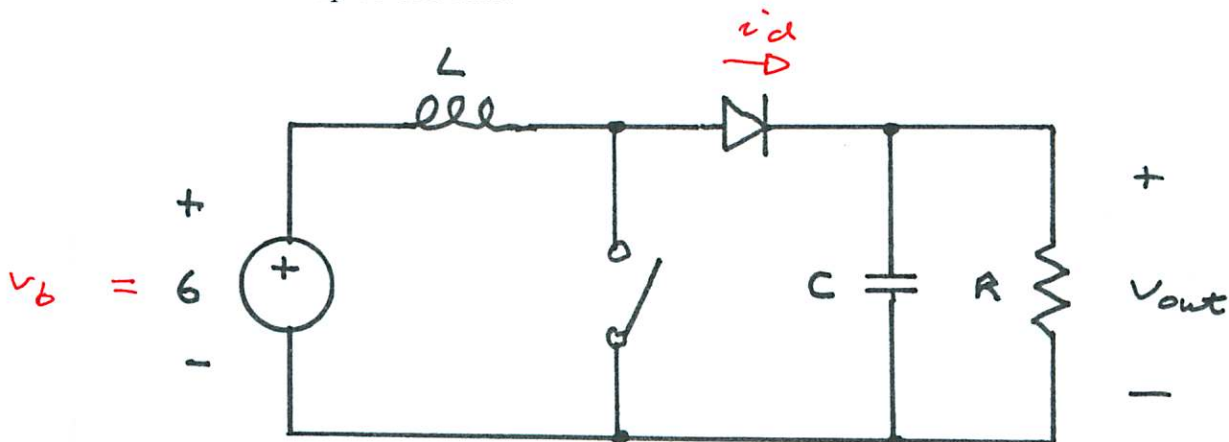Problem 2

The boost converter drawn below is intended to operate with $v_{out} = 10$ V subject to a 100-kHz switching frequency. An acceptable design will deliver a load current up to 500 mA.



A. Specify the duty cycle D .

$$10 = \frac{6}{1-D} \rightarrow D = 0.4$$

B. Specify a reasonable design value for C .

worst case $R = \frac{10}{0.5} = 20 \Omega$

$$RC \sim 10T \xrightarrow{1/f} C = \frac{10 \times 10^{-5}}{20} = 5 \mu F$$

C. Specify L so that the minimum inductor current is just barely positive at all times (continuous mode).

$$L = \frac{v_b D(1-D)T}{2 \times \text{dc load current}} = \frac{6(0.4)(0.6) \times 10^{-5}}{1} = 14.4 \mu H$$

D. Specify the maximum diode current subject to the conditions of part C.

$$i_d(\max) = \frac{2v_b}{(1-D)^2 R} = \frac{2 \times 6}{(0.6)^2 \cdot 20} = 1.67 A$$


Problem 3

The circuit drawn below features a Zener diode with $V_z = 12\text{ V}$. The voltage source V_s varies according to the relation

$$V_s(t) = 15[1 + \cos 100\omega t].$$

$$\left\{ \begin{array}{l} V_s(\max) = 30 \\ V_s(\min) = 0 \end{array} \right.$$

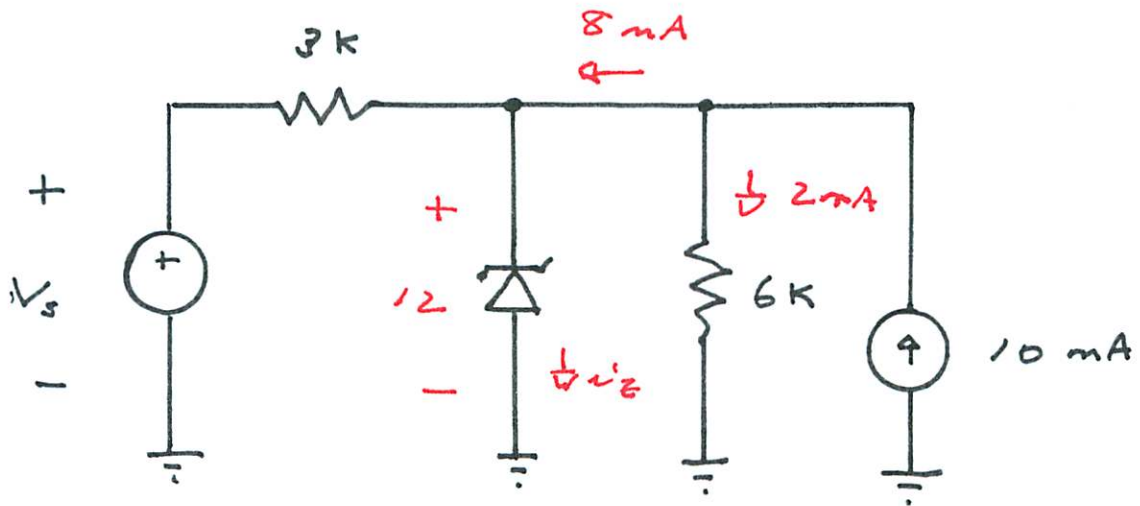Determine the range of instantaneous power that the Zener diode absorbs.



$$V_s = 30\text{ V} \rightarrow i_z = 8\text{ mA} + \frac{30 - 12}{3} = 14\text{ mA}$$

$$P_z = 12\text{ V} \times 14\text{ mA} = 168\text{ mW}$$

$$V_s = 0 \rightarrow i_z = 8\text{ mA} + \frac{0 - 12}{3} = 4\text{ mA}$$


$$P_z = 12\text{ V} \times 4\text{ mA} = 48\text{ mW}$$

$$48\text{ mW} < P_z < 168\text{ mW}$$

Problem 4

The BJTs have $\beta_F = 100$.


Determine R such that $v_{out} = -3$ V.

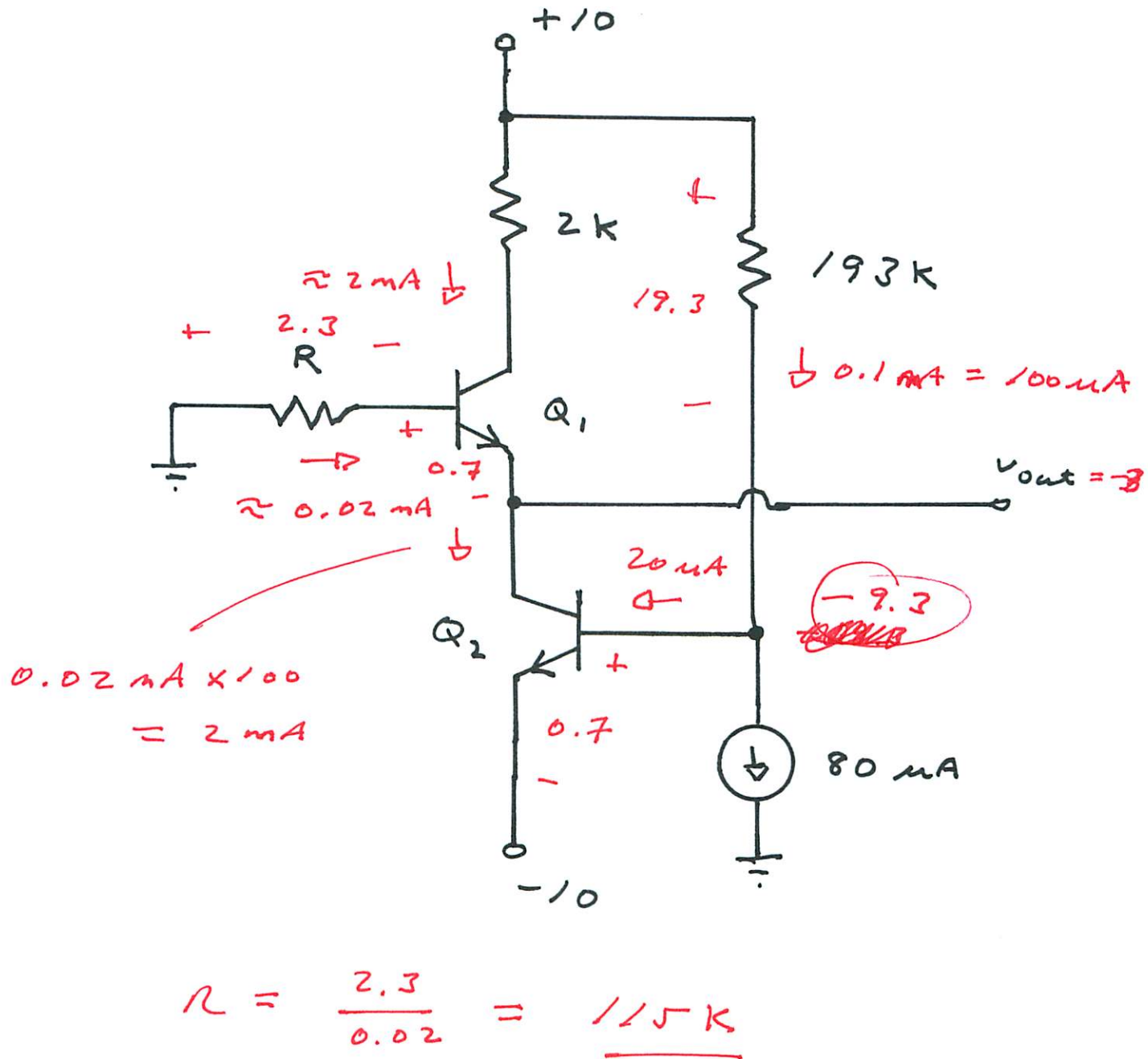

Problem 5

The MOSFETs have $K'W/L = 2 \text{ mA/V}^2$ and $|V_T| = 1 \text{ V}$.

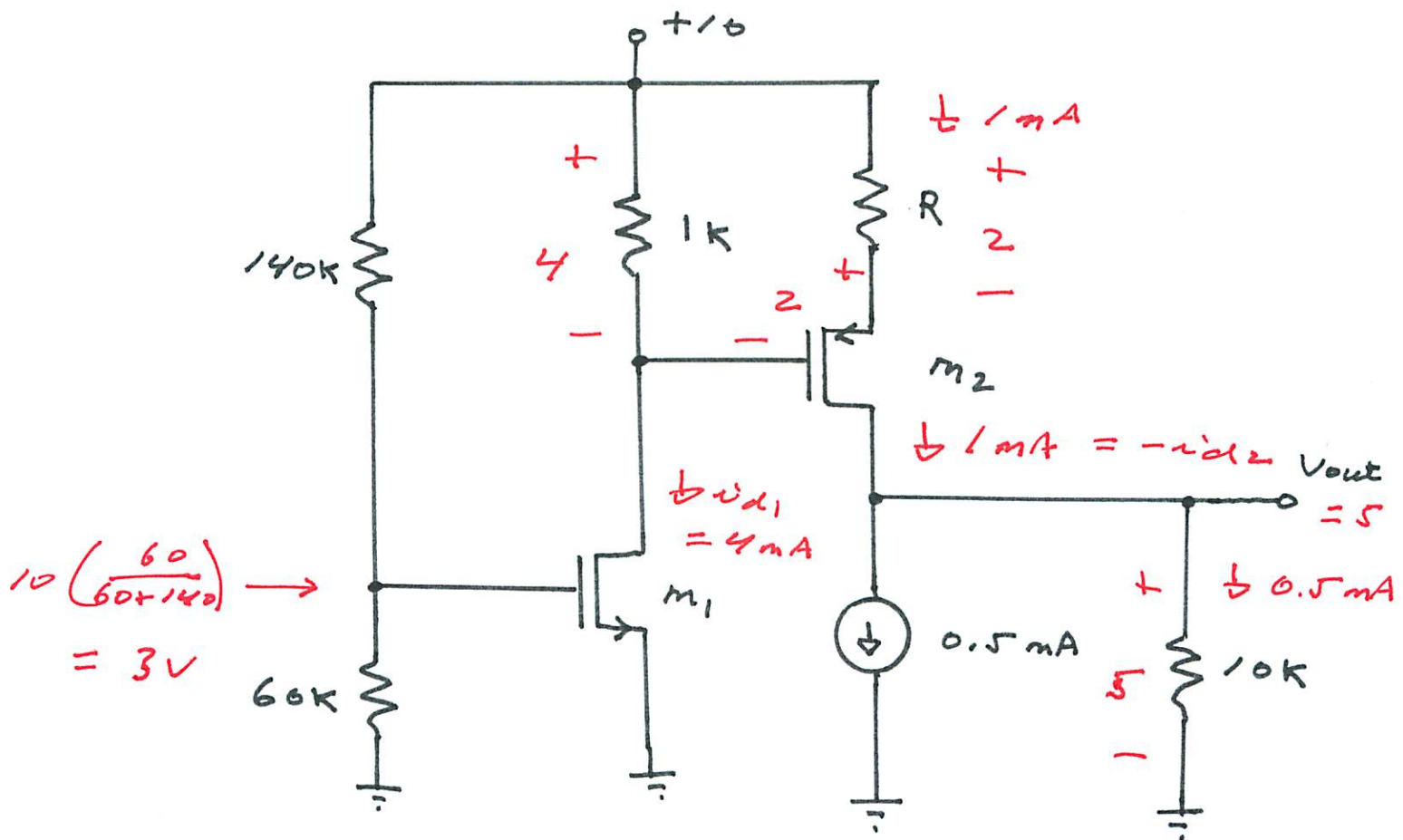Find R such that $v_{out} = 5 \text{ V}$.



$$v_{ds1} = \frac{1}{2} (2) (3-1)^2 = 4\text{mA}$$

$$-i_{d2} = 1\text{mA} = \frac{1}{2} (2) (v_{gs2} + 1)^2$$

$$v_{gs2} = -2 \rightarrow v_{sg2} = +2$$

$$R = \frac{2}{1\text{mA}} = \underline{2\text{k}\Omega}$$