

Design of a Pipelined 3-Element Adder

Lab 7 P1 + P2

Introduction

10 / 16 / 2012

Our focus of this discussion is design and paper submission.

Verilog coding and simulation is not discussed.

So skip pages 3, 4, 8, & 9 of the 12-page document.

$(\$R) \leq (\$Z) + (\$Y) + (\$X)$ if there is no overflow.

4-bit Reg IDs because it is a

16x16 IFRF



Read PORTS



Write Port

Initial contents of the Register File

Register id			Content
Register 00	0		0001h
Register 01	1		0002h
Register 02	2		0004h
Register 03	3		0008h
Register 04	4		0010h
Register 05	5		0020h
Register 06	6		0040h
Register 07	7		0080h

Register id			Content
Register 08	8		0100h
Register 09	9		0200h
Register 10	A		0400h
Register 11	B		0800h
Register 12	C		1000h
Register 13	D		2000h
Register 14	E		FFF8h
Register 15	F		FFFFh

~~\$0~~
is like
any other
register.

Instr. format

32 bits

RUN

R

Z

Y

X



1 = add

15

4

4

4

4



O = NOP

Add \$4, \$3, \$2, \$1 ; Translation: 80004321 (Hex)

Dependent instruction

Can only get help from

The Senior in



Senior is in a position to
help a junior only when the

Senior is in



Dependent junior can only

Stall in



(a) Text book 5 - stage pipeline

(b) This special pipeline



What if There is only one
Source register (like in Lab 7 P3)?

Can the dependent Instr. Stall in

EX1?







Question from Lab 7 P3

_____ (Unlike/Like) the MIPS 5 stage pipeline, where the instructions _____ (have only one source register / can have two source registers), here the instructions _____ (have only one source register / can have two source registers). Hence it _____ (is / isn't) possible to stall the dependent instruction in EX1 stage instead of the ID stage.

 Q 1.7 2 of 2 to 1 muxes $\Rightarrow$ 1 of 3 to 1 mux




 


1. Complete all missing connections marked in dotted lines . Also complete the RA(Result Addressee) connection in ID stage (ID_RA).
2. Complete all five enable (EN) controls on the pipeline registers (including PC).
3. Complete the forwarding paths into the four forwarding muxes.
4. Complete logic to inject bubble into the next stage if the current instruction is being stalled or being flushed.
5. Draw the logic on a separate page for generating STALL, X_FORW1, Y_FORW1, Z_FORW1, Z_FORW2.

Pinelined 3-element Adder **Block Diagram** **LAB 7 Part1**

Fig. 1

 

 ee457_lab7_P1_comparator_inference_signal_naming_convention.pdf



EX2 WB

Part 2


Combined into


EX2 WB

We provided an incomplete block diagram for this part on the last page. We just removed the EX2/WB stage register (of the Part 1) but did not fix anything else. You please remove items which are not needed and complete the rest of this block diagram.

Though we are not doing timing design, let us apply this simple rule regarding helping (forwarding) towards the end of the clock. The register file is internally forwarding and we assume that the clock is wide enough for the instruction in EX2WB stage to perform the original EX2 operation of adding Z, checking to see if there was an overflow, and writing into the register file and forwarding the result data (write data) at the end of the clock to the instruction in the ID stage.

 Question 2.1 If that is the case, the instruction in EX2WB stage should not have any difficulty to help the instruction in EX1 towards the end of the clock for the _____ (X / Y / Z) register as the recipient of the help does not have to perform any addition operation on this data.



 

This figure is basically the same as the Fig. 1 for part 1 on page 2 except that the EX2/WB stage register was removed as we are merging the EX2 and WB stages into one EX2WB stage. You need to remove items which are not necessary and complete the rest.. **You need to generate any STALL and/or FORW (forwarding) signals on this page itself.**

Pinelined 3-element Adder **Block Diagram** **LAB 7 Part2 (with EX2 and WB merged)**

Fig. 2

