

## Circuits for driving DIP relays

The circuits below can be used to control one of the DIP relays available for EE459 projects. If the microcontroller or gate can source or sink about 3ma either can be used. For TTL gates that can only sink this much current, the circuit with the PNP transistor should be used.

